

## UNIT IV


### FREQUENCY ANALYSIS OF BJT AND MOSFET AMPLIFIERS

#### 4.1. Hybrid – $\Pi$ model:

At low frequencies we analyse transistor using h-parameters. But for high frequency analysis the h-parameter model is not suitable for following reasons.

1. The values of h-parameters are not constant at high frequencies. Therefore, it is necessary to analyse transistor at each and every frequency, which is impracticable.
2. At high frequency h-parameters becomes more complex in nature.

##### 4.1.1. Elements in the Hybrid – $\Pi$ model:

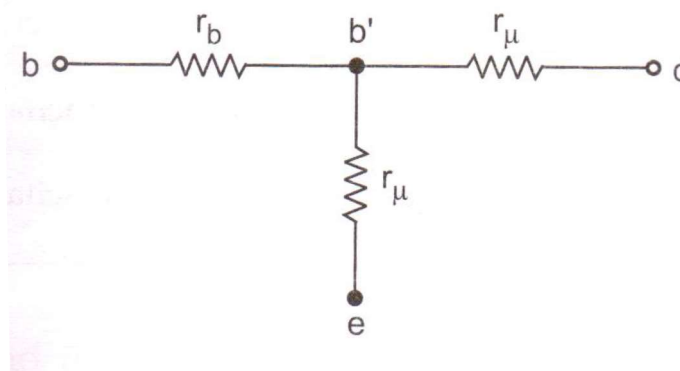

**Fig 4.1. Virtual base**

i)  $C_{\pi}$  and  $C_{\mu}$ : The diffusion capacitance  $C_{\pi}$  connected between  $b'$  and  $e$  represents the excess minority carrier storage in the base. The capacitive effect of normally forward biased base-emitter junction of the transistor is represented by  $C_{\pi}$  in the Hybrid –  $\Pi$  model. The reverse bias PN junction exhibits a capacitive effect called the transition capacitance. This capacitive effect of normally reverse biased collector base junction of the transistor is represented by  $C_{\mu}$  in the Hybrid –  $\Pi$ .

ii)  $r_b$ : The bulk resistance between external base terminal and internal node  $b'$  is represented as  $r_b$ . This resistance is called as base spreading resistance.

iii)  $r_{\pi}$ : The resistance  $r_{\pi}$  is that portion of the base emitter which may be thought of as being in series with the collector junction. This establishes a virtual base  $b'$  for the junction capacitances to be connected to instead of  $b$ .

iv)  $r_\mu$ : Due to early effect, the varying voltages across the collector to emitter junction results in both results in base-width modulation. A change in the effective base width causes the emitter current to change. This feedback effect between output and input is taken into account by connecting  $r_\mu$  between  $b'$  and  $c$ .

v)  $g_m$ : Due to the small changes in voltage  $V_\pi$  across the emitter junction, there is excess-minority carrier concentration injected into the base which is proportional to the  $V_\pi$ . Therefore, resulting small signal collector current, with collector shorted to the emitter is also proportional to the emitter is proportional to the  $V_\pi$ . This effect accounts for the current generator  $g_m V_\pi$ .  $g_m$  is called transconductance.

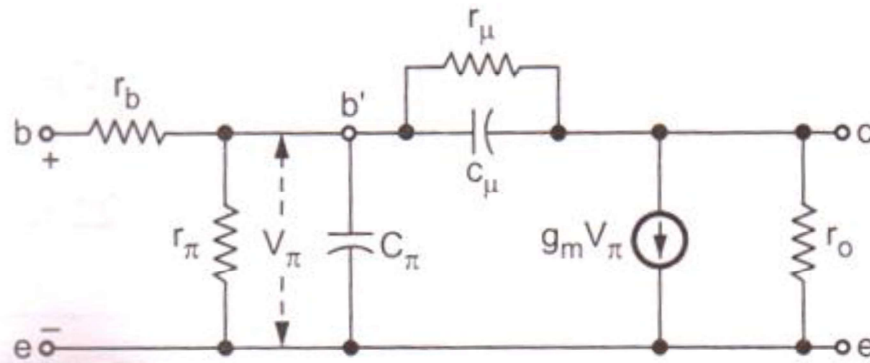


Fig 4.2. Hybrid –  $\Pi$  model for a transistors in the CE configuration

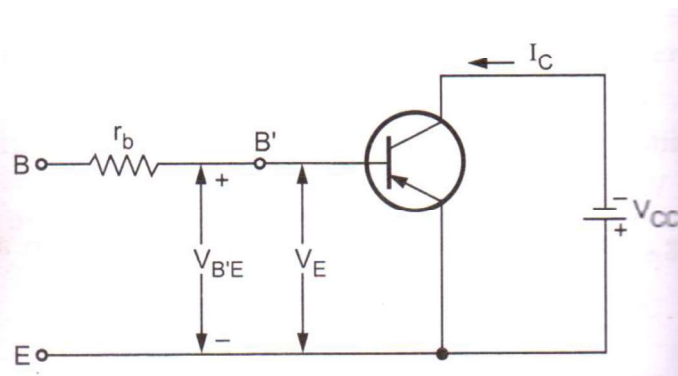


Fig 4.3. Pertaining to the derivation of  $g_m$

i) **Transconductance ( $g_m$ ):**

$$g_m = \left. \frac{\partial I_C}{\partial V_{B'E}} \right|_{V_{CE}}$$

The collector current in active region is given as,

$$I_C = I_{CO} - \alpha I_E$$

And therefore

$$\partial I_C = -\alpha \partial I_E \quad \because I_{CO} = \text{constant}$$

Sub  $\partial I_C$  in  $g_m$ ,

$$g_m \equiv \alpha \frac{\partial I_E}{\partial V_{B'E}} \propto \frac{\partial I_E}{\partial V_E} \quad \because V_E = V_{B'E}$$

The emitter diode resistance,

$$r_e = \frac{\partial V_E}{\partial I_E}$$

Sub  $r_e$  in  $g_m$ ,

$$g_m = \frac{\alpha}{r_e}$$

The dynamic resistance is given as,

$$r_e = \frac{V_T}{I_E}$$

$$V_T = \frac{KT}{q}$$

where, Boltzmann constant,  $K = 1.38 \times 10^{-23} \text{ J/}^\circ\text{K}$

electronic charge,  $q = 1.6 \times 10^{-19} \text{ C}$

Sub  $r_e$  in  $g_m$

$$g_m = \frac{\alpha I_E}{V_T} = \frac{I_{CO} - I_C}{V_T} \quad \because I_C = I_{CO} - \alpha I_E$$

For npn transistor,

$$g_m = \frac{I_C - I_{CO}}{V_T}$$

$$g_m = \frac{I_c}{V_T} = \frac{I_c q}{K_T} = \frac{I_c}{\frac{1.38 \times 10^{-23}}{1.6 \times 10^{-19}} \times 300}$$

$$g_m = \frac{|I_c| \text{mA}}{26 \text{mV}}$$

ii) Input conductance,  $g_{b'e}$ :

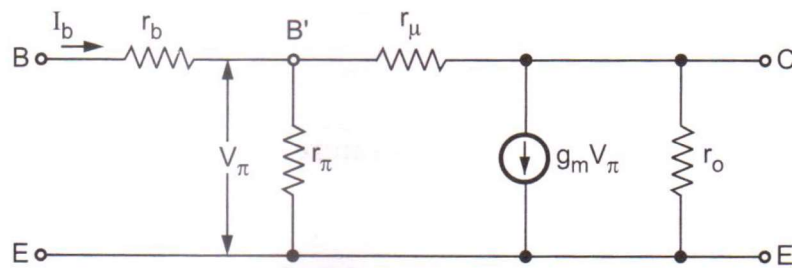


Fig 4.4. Hybrid – Π model for CE configuration at low frequency

The short circuit current gain  $h_{fe}$  is defined as,

$$h_{fe} = \frac{I_c}{I_b} \dots \dots \dots (1)$$

$$I_c = g_m V_\pi$$

$$= g_m I_b r_\pi \quad \because V_\pi = I_b r_\pi$$

$$\frac{I_c}{I_b} = g_m r_\pi \dots \dots \dots (2)$$

Compare (1) & (2)  $h_{fe} = g_m r_\pi$

$$r_\pi = \frac{h_{fe}}{g_m}$$

$$g_{b'e} = \frac{g_m}{h_{fe}} \quad \therefore \frac{1}{r_\pi} = g_{b'e}$$

$$\text{W.K.T, } g_m = \frac{I_c}{V_T}$$

$$r_\pi = \frac{h_{fe} V_T}{|I_c|}$$

$$g_{b'e} = \frac{|I_c|}{V_T h_{fe}}$$

iii) The feedback conductance ,  $g_{b'c}$ :

Input open circuit,

$$V_i = h_{re} V_{ce}$$

$$V_{ce} = I_1 (r_\mu + r_\pi)$$

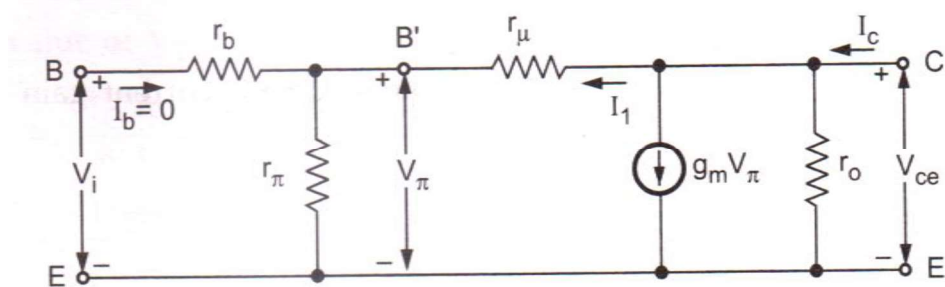


Fig 4.5. Hybrid – Π model for CE configuration

$$I_1 = \frac{V_{ce}}{r_\mu + r_\pi}$$

$$V_\pi = I_1 r_\pi$$

$$\text{With } I_b = 0, \quad V_i = V_\pi$$

Sub  $I_1$  in  $V_\pi$ ,

$$V_i = V_\pi = \frac{V_{ce}}{r_\mu + r_\pi} r_\pi$$

Compare both  $V_i$  equation,

$$h_{re} V_{ce} = \frac{r_\pi V_{ce}}{r_\mu + r_\pi}$$

$$h_{re} = \frac{r_\pi}{r_\mu + r_\pi}$$

$$r_\pi = h_{re} r_\mu + h_{re} r_\pi$$

$$r_\pi - h_{re} r_\pi = h_{re} r_\mu$$

$$r_{\pi} (1 - h_{re}) = h_{re} r_{\mu}$$

$$r_{\mu} = \left( \frac{1 - h_{re}}{h_{re}} \right) r_{\pi} \quad \because 1 - h_{re} \approx 1$$

$$r_{\pi} = \frac{r_{\mu}}{h_{re}}$$

$$g_{b'c} = \frac{h_{re}}{r_{\pi}} = h_{re} g_{b'c}$$

$$g_{b'c} = \frac{h_{re} |I_C|}{h_{re} V_T} \quad \because g_{b'c} = \frac{|I_C|}{h_{re} V_T}$$

**iv) Base spreading resistance,  $r_b$ :**

Output shorted,

$$h_{ie} = r_b + r_{\pi}$$

$$r_b = h_{ie} - r_{\pi}$$

$$r_b = h_{ie} - \frac{h_{fe} V_T}{|I_C|} \quad \therefore r_{\pi} = \frac{h_{fe} V_T}{|I_C|}$$

**v) Output conductance,  $g_{ce}$ :**

The output conductance,

$$h_{oe} = \frac{I_C}{V_{ce}}$$

Applying KCL to the output circuit,

$$I_C = \frac{V_{ce}}{r_o} + g_m \left( \frac{r_{\pi} V_{ce}}{r_{\pi} + r_{\mu}} \right) + \frac{V_{ce}}{r_{\mu} + r_{\pi}}$$

$$\frac{I_C}{V_{ce}} = \frac{1}{r_o} + \frac{g_m r_{\pi}}{r_{\pi} + r_{\mu}} + \frac{1}{r_{\mu} + r_{\pi}} \quad \therefore h_{fe} = g_m r_{\pi}$$

$$h_{oe} = \frac{1}{r_o} + \frac{h_{fe}}{r_{\pi} + r_{\mu}} + \frac{1}{r_{\pi} + r_{\mu}}$$

$$h_{oe} = \frac{1}{r_o} + \frac{(h_{fe} + 1)}{r_{\pi} + r_{\mu}}$$

$$= \frac{1}{r_o} + \frac{h_{fe}}{r_{\pi} + r_{\mu}} \quad \therefore h_{fe} \gg 1$$

$$h_{oe} = \frac{1}{r_o} + \frac{h_{fe}}{r_{\mu}} \quad \therefore r_{\mu} \gg r_{\pi}$$


$$h_{oe} = g_{ce} + g_b' h_{fe}$$

$$\frac{1}{r_{ce}} = g_{ce} = h_{oe} - g_b' h_{fe}$$

#### 4.2. General shape of frequency response of amplifiers:

Let us consider an audio frequency amplifier which operates over audio frequency range extending from 20Hz to 20KHz. The audio frequency amplifier are used in radio receivers, to address large public meeting, annual social gathering of college, for various announcements to be made for passenger on railway platforms, etc.

An amplifier should ideally provide the same amplification for all frequencies. The degree to which this is done is usually indicated by a curve known as frequency response curve of the amplifier.

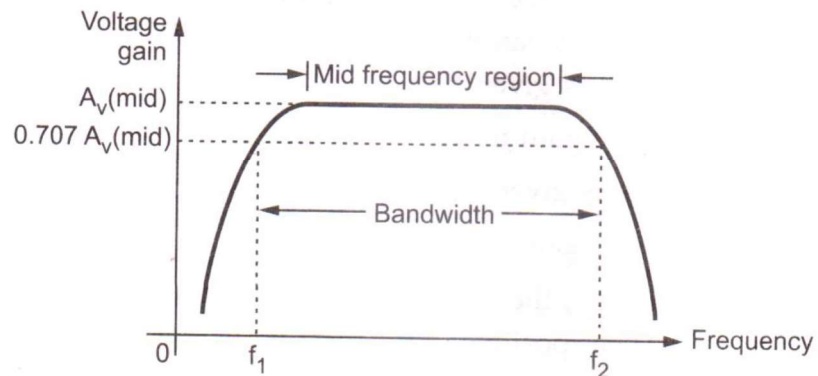

**Fig 4.6. A typical frequency response of an amplifier**


To plot this curve, input voltage to the amplifier is kept constant & frequency of input signal is continuously varied. It is seen from the frequency response curve of an audio frequency amplifier that the gain of the amplifier remains fairly constant in the mid freq range, while the gain varies with frequency in low & high freq regions on the curve. The decrease in voltage gain with frequency is called roll off.

Bandwidth of the amplifier is defined as the difference between  $f_2$  and  $f_1$ .

$$B.W = f_2 - f_1$$

#### 4.3. Significance of octaves & decodes:

1. The octaves & decodes are the measure of change in frequency.
2. A ten times change in frequency is called decode.
3. An octaves corresponds to a doubling or halving of the frequency.
4. For example an increase in frequency from 100Hz to 200Hz is an octave. Likewise, a decrease in freq from 100Hz to 50Hz is also an octave.

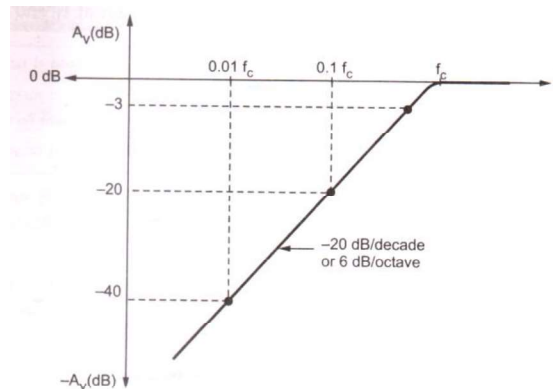

**Fig 4.7. Frequency response showing significance of decade and octave**

The voltage gain of the amplifier outside the midband is approximately given as,

$$A = \frac{A_{\text{mid}}}{\sqrt{1 + (f_1/f)^2} \sqrt{1 + (f/f_2)^2}}$$

**i) Midband :**

$$A = A_{\text{mid}}$$

**ii) Below Midband:**

$$A = \frac{A_{\text{mid}}}{\sqrt{1 + \left(\frac{f_1}{f}\right)^2}}$$

**iii) Above Midband:**

$$A = \frac{A_{\text{mid}}}{\sqrt{1 + \left(\frac{f}{f_2}\right)^2}}$$



#### 4.4. Effect of various capacitors on frequency response:

##### 4.4.1. Effect of coupling capacitors:

1. Reactance of a capacitors,  $X_C = \frac{1}{2\pi f_c}$
2. At medium & high frequencies, the factor  $f$  makes  $X_C$  very small, so that all coupling capacitor behave as short circuits.
3. At low frequencies,  $X_C$  increases. This increase in  $X_C$  drops the signal voltage across the capacitor & reduce the circuit gain.

##### 4.4.2. Effect of bypass capacitors:

1. At lower frequencies, the bypass capacitors  $C_E$  is not a short. so the emitter is not ac ground.
2.  $X_C$  in parallel with  $R_E$  ( $R_S$  in case of FET) creates an impedance.
3. The signal voltage drops across this impedance reducing the circuit gain.

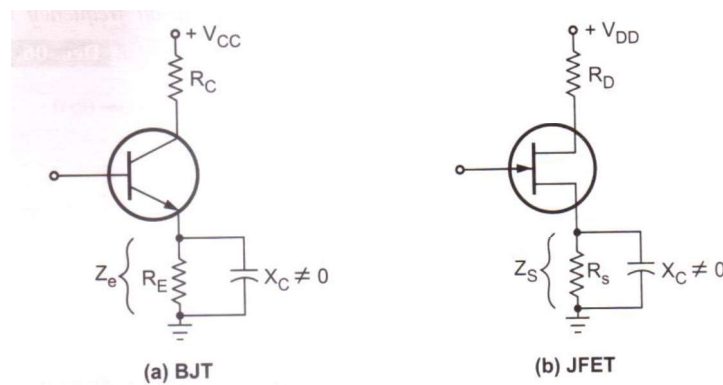


Fig 4.8. At low frequencies emitter (source in case of FET) is not at ac ground

##### 4.4.3. Effect of internal transistor capacitors:

1. At high frequencies, the coupling and bypass capacitors act as short circuit & do not affect the amplifier frequency response.
2. However, at high frequencies, the internal capacitances, commonly known as junction capacitances, reducing the circuit gain.
3. At higher frequencies, the reactances of the junction capacitances are low. As frequency increases, the reactances of junction capacitances fall.
4. When these reactances become small enough, they provide shunting effect as they are in parallel with junction. This reduces the circuit gain & hence the output voltage.

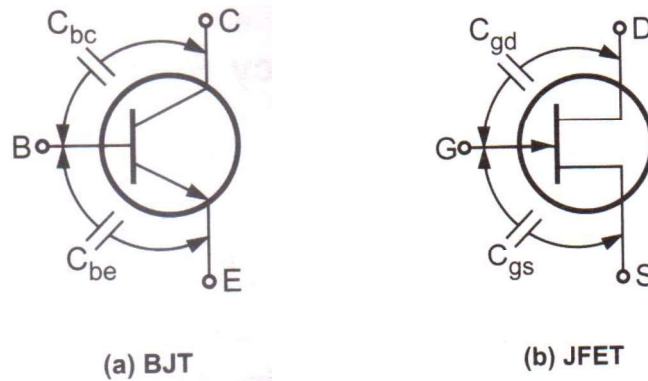


Fig 4.9. Internal transistor capacitances

#### 4.5. Miller theorem:

In transistor amplifier it is necessary to split the capacitance between input & the output. This can be achieved using Miller's theorem.

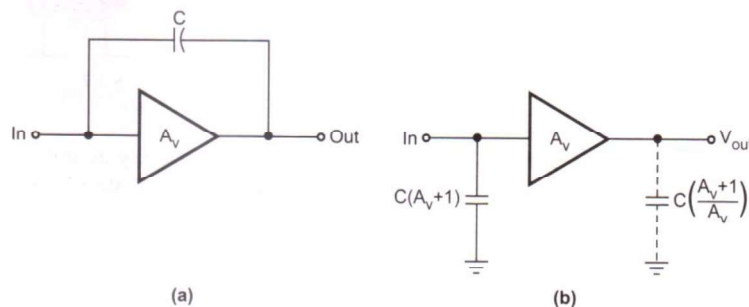


Fig 4.10. Splitting of capacitor using Miller's theorem

#### 4.6. Low Frequency analysis of BJT:

The amplifier has three RC networks that affect its gain as the frequency is reduced below midrange these are,

- i) RC networks formed by the input coupling capacitor  $C_1$  & the input impedance of the amplifier.
- ii) RC networks formed by the output coupling capacitor  $C_2$ , the resistance looking in at the collector & the load resistance.

iii) RC networks formed by the emitter bypass capacitor  $C_E$  & the resistance looking in at the emitter.

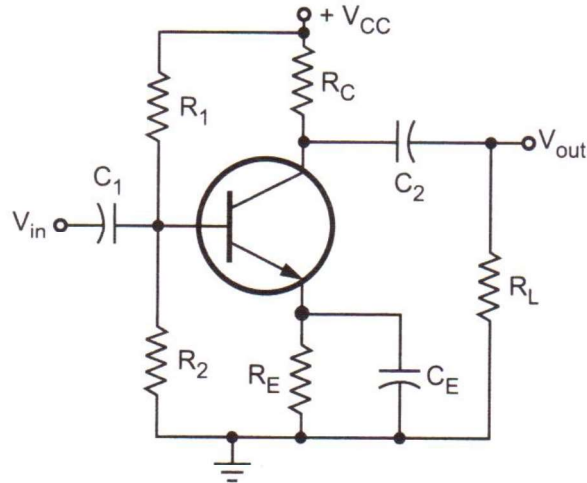


Fig 4.11. Typical RC coupled CE amplifier

#### 4.6.1. Input RC network:

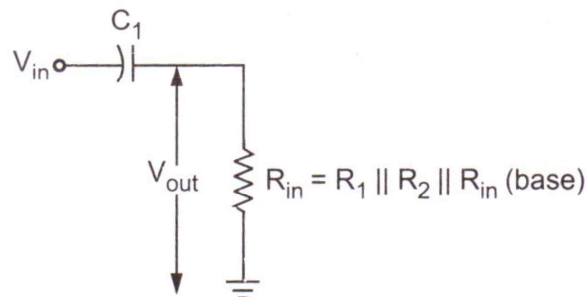


Fig 4.12. Input RC network formed by  $C_1$

Applying voltage divider theorem,

$$V_{out} = \left( \frac{R_{in}}{\sqrt{R_{in}^2 + X_{C1}^2}} \right) V_{in}$$

$$V_{out} = 0.707 V_{in}$$

$$0.707 V_{in} = \left( \frac{R_{in}}{\sqrt{R_{in}^2 + X_{C1}^2}} \right) V_{in}$$

$$\frac{R_{in}}{\sqrt{R_{in}^2 + X_{C1}^2}} = 0.707 = 1/\sqrt{2}$$

The reduction in overall gain is given by,

$$A_v = 20 \log \left( \frac{V_{out}}{V_{in}} \right)$$

$$= 20 \log (0.707) = -3\text{dB}$$

The frequency  $f_c$  at this condition is called lower critical frequency & is given by,

$$f_c = \frac{1}{2\pi R_{in} C_1}$$

$$\text{where } R_{in} = R_1 \parallel R_2 \parallel h_{ie}$$

$$f_c = \frac{1}{2\pi (R_1 \parallel R_2 \parallel h_{ie}) C_1}$$

If the resistance of the input source is taken into account,

$$f_c = \frac{1}{2\pi (R_S + R_{in}) C_1}$$

The phase angle in an input RC circuit is expressed as,

$$\theta = \tan^{-1} \left( \frac{X_{C1}}{R_{in}} \right)$$

#### 4.6.2. Output RC network:

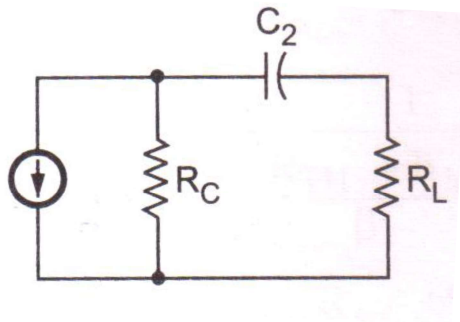


Fig 4.13. Current source

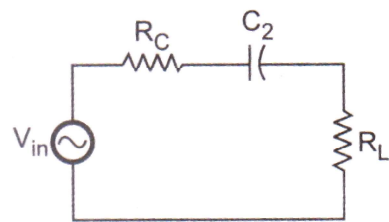


Fig 4.14. Current source replaced by voltage source

The critical frequency source for this RC network is given by,

$$f_c = \frac{1}{2\pi(R_C + R_L)C_2}$$

The phase angle in the output RC circuit is expressed as,

$$\theta = \tan^{-1} \left( \frac{X_{C2}}{R_C + R_L} \right)$$

#### 4.6.3. Bypass Network:

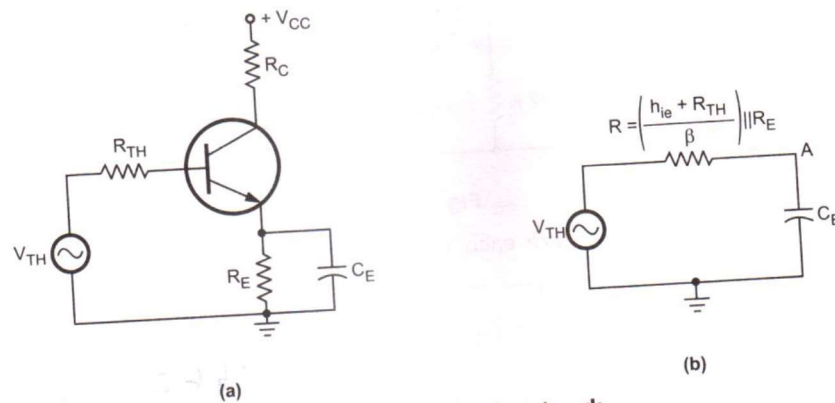


Fig 4.15. Bypass RC Network

The critical frequency for the bypass network is,

$$f_c = \frac{1}{2\pi R C_E}$$

$$f_c = \frac{1}{2\pi \left[ \left( \frac{h_{ie} + R_{TH}}{\beta} \right) \parallel R_E \right] C_E}$$

#### 4.7. CE short circuit current gain using hybrid $\pi$ model:


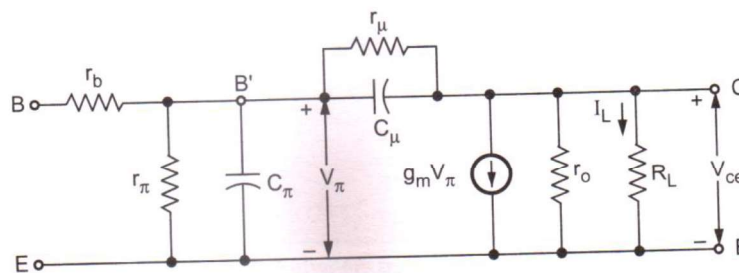


Fig 4.16. Bypass RC Network

Output short circuited  $r_o$  becomes zero,  $r_\pi$  &  $C_\pi$  &  $C_\mu$  appear in parallel. As  $r_\mu \gg r_\pi$ ,  $r_\mu$  is neglected with these approximation we get simplified hybrid  $\pi$  model for short circuit CE transistor.

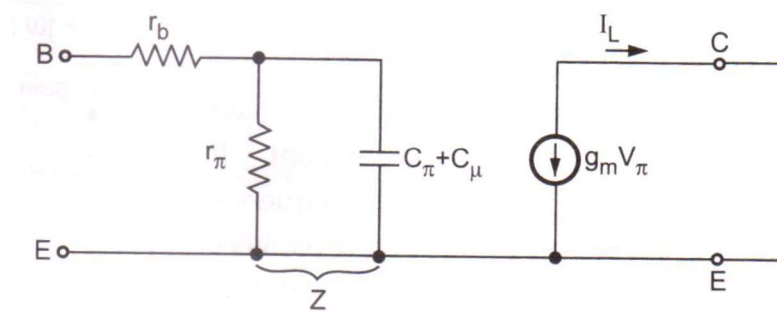


**Fig 4.17. Simplified hybrid  $\pi$  model for short circuit CE transistor**

Parallel combination of  $r_\pi$  &  $(c_\pi + c_\mu)$  is given as,

$$Z = \frac{r_\pi \times \frac{1}{j\omega(c_\pi + c_\mu)}}{r_\pi + \frac{1}{j\omega(c_\pi + c_\mu)}}$$

$$= \frac{r_\pi \times \frac{1}{j\omega(c_\pi + c_\mu)}}{\frac{j\omega r_\pi(c_\pi + c_\mu) + 1}{j\omega(c_\pi + c_\mu)}}$$

$$Z = \frac{r_\pi}{1 + j\omega r_\pi(c_\pi + c_\mu)}$$

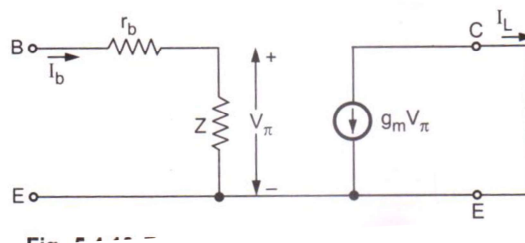

**Fig 4.18. Further simplified hybrid  $\pi$  model**

$$V_{\pi} = I_b Z$$

$$Z = \frac{V_{\pi}}{I_b}$$

$$A_i = \frac{I_L}{I_b}$$


$$= \frac{-g_m V_{\pi}}{I_b} \quad \therefore Z = \frac{V_{\pi}}{I_b}$$

$$= -g_m Z$$

$$A_i = \frac{-g_m r_{\pi}}{1 + j\omega r_{\pi}(c_{\pi} + c_{\mu})} \quad \therefore h_{fe} = g_m r_{\pi}$$

$$A_i = \frac{-h_{fe}}{1 + j\omega r_{\pi}(c_{\pi} + c_{\mu})}$$

1. The current is not constant .If depends on frequency.
2. When frequency increases,  $A_i$  reduces current gain.

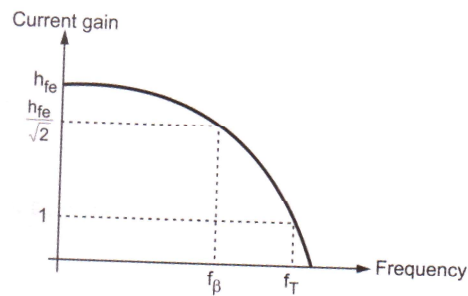

**Fig 4.19. Frequency response of CE short circuit**

$$f_{\beta} = \frac{1}{2\pi r_{\pi}(c_{\pi} + c_{\mu})}$$

Sub  $f_{\beta}$  in  $A_i$  ,

$$A_i = \frac{-h_{fe}}{1 + j \frac{f}{f_{\beta}}}$$

$$|A_i| = \frac{h_{fe}}{\sqrt{1 + \left(\frac{f}{f_\beta}\right)^2}}$$

$$\text{At } f = f_\beta$$

$$|A_i| = \frac{h_{fe}}{\sqrt{2}}$$

**i)  $f_\beta$  (cut off frequency):**

It is the frequency at which the transistor's short circuit CE current gain drops by 3dB or  $\frac{1}{\sqrt{2}}$  times from its value at low frequency. It is given by,

$$f_\beta = \frac{1}{2\pi r_\pi (c_\pi + c_\mu)}$$

$$f_\beta = \frac{g_{b'e}}{2\pi (c_\pi + c_\mu)}$$

$$f_\beta = \frac{g_m}{2\pi h_{fe} (c_\pi + c_\mu)} \because g_{b'e} = \frac{1}{r_\pi} = \frac{g_m}{h_{fe}}$$

**ii)  $f_\alpha$  (cut off frequency):**

It is the frequency at which the transistor's short circuit CB current gain drops by 3 dB or  $1/\sqrt{2}$  times from its value at low frequency. The expression for  $f_\alpha$  can be derived in the similar manner as for  $f_\beta$ .

The current gain for CB configuration is given as,

$$f_\alpha = \frac{1}{2\pi r_\pi (1 + h_{fb}) c_\pi}$$

$$f_\alpha = \frac{1 + h_{fe}}{2\pi r_\pi c_\pi} \approx \frac{h_{fe}}{2\pi r_\pi c_\pi}$$

$$|A_i| = \frac{h_{fb}}{\sqrt{1 + \left(\frac{f}{f_\alpha}\right)^2}}$$

$$A_i f = f_\alpha$$

$$|A_i| = \frac{h_{fb}}{\sqrt{2}}$$



iii)  $F_T$  : It is the frequency at which short circuit cE current gain becomes unity.

$$A_i \quad f = f_T, |A_i| = 1$$

$$1 = \frac{h_{fe}}{\sqrt{1 + \left(\frac{f_T}{f_\beta}\right)^2}}$$

$$h_{fe} = \sqrt{1 + \left(\frac{f_T}{f_\beta}\right)^2}$$

$$h_{fe} = \frac{f_T}{f_\beta} \quad \because \frac{f_T}{f_\beta} \gg 1$$

$$f_T = f_\beta h_{fe}$$

Sub  $f_\beta$  in  $f_T$ ,

$$f_T = \frac{h_{fe} \times g_m}{h_{fe} 2\pi (C_\pi + C_\mu)}$$

$$f_T = \frac{g_m}{2\pi (C_\pi + C_\mu)}$$

Since  $C_\pi \gg C_\mu$ ,

$$f_T = \frac{g_m}{2\pi C_\pi}$$

#### 4.8. Internal capacitance of MOSFET & high frequency model:

High frequency response of MOSFET affects due to internal capacitances. There are two types of internal capacitances in the MOSFET.

**i) Gate capacitance:** It is a parallel plate capacitance formed by a gate electrode with the channel, with the oxide layer acts as a capacitor dielectric .It is denoted as  $C_{ox}$ .

**ii) Junction capacitance:** (Source-body & drain-body depletion layer capacitances)

These capacitances are due to the reverse biased pn junctions formed by the  $n^+$  drain & the p type substrate & the  $n^+$  drain region and the p-type substrate. These are denoted as source diffusion capacitance & drain diffusion capacitance, respectively.

##### 4.8.1. Gate capacitances:

There are three gate capacitances:  $C_{gs}$ ,  $C_{gd}$  &  $C_{gb}$ .

In triode region the channel as uniform depth & hence we have,

$$C_{gs} = C_{gd} = \frac{1}{2} WL C_{ox}$$

In saturation region ,

$$C_{gs} = \frac{2}{3} WL C_{ox}$$

$$C_{gd} = 0$$

In cut off region,

$$C_{gs} = C_{gd} = 0$$

Gate-body model capacitance is given by,

$$C_{gb} = WL C_{ox} \quad (\text{cut off})$$

The overlap capacitance,

$$C_{ov} = WL_{ov} C_{ox}$$

Where,  $L_{ov}$  - overlap length & is typically 0.05L to 0.1L

#### 4.8.2. Junction capacitances:

Source diffusion capacitance,

$$C_{sb} = \frac{C_{sbo}}{\sqrt{1 + \frac{V_{SB}}{V_o}}}$$

Where,  $C_{sbo}$  -value of  $C_{sb}$  at zero body –source bias.

$V_{SB}$  -mangnitude of the reverse bias voltage.

$V_o$  -junction built in voltage, typically 0.6v to 0.8v.

The drain diffusion capacitance,

$$C_{db} = \frac{C_{dbo}}{\sqrt{1 + \frac{V_{DB}}{V_o}}}$$

#### 4.8.3. Unity gain frequency:

The  $f_T$  is the frequency at which the short circuit current gain of the CS MOSFET amplifier becomes unity. Output terminals are shorted.

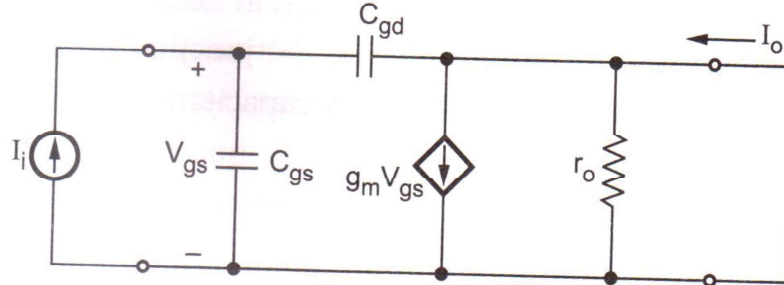


Fig 4.20. High frequency model to determine short-circuit current gain

$$I_o \approx g_m V_{gs}$$

$V_{gs}$  in terms of  $I_i$ ,

$$V_{gs} = \frac{I_i}{s(C_{gs} + C_{gd})}$$

$$I_i = V_{gs} s(C_{gs} + C_{gd})$$

$$|A_i| = \frac{I_o}{I_i} = \frac{g_m V_{gs}}{V_{gs} s(C_{gs} + C_{gd})} = \frac{g_m}{s(C_{gs} + C_{gd})}$$

$$f_T \rightarrow |A_i| = 1$$

$$\omega_T = \frac{g_m}{(C_{gs} + C_{gd})}$$

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

#### 4.9. Frequency response of CS amplifier:

$$V_o = I_L R_L' = g_m V_{gs} R_L'$$

$$\text{Where, } R_L' = r_o || R_D || R_L$$

By Miller's theorem,

$$C_{eq} = (1 + A_v)C$$

$$C_{eq} = (1 + A_v)C_{gd}$$

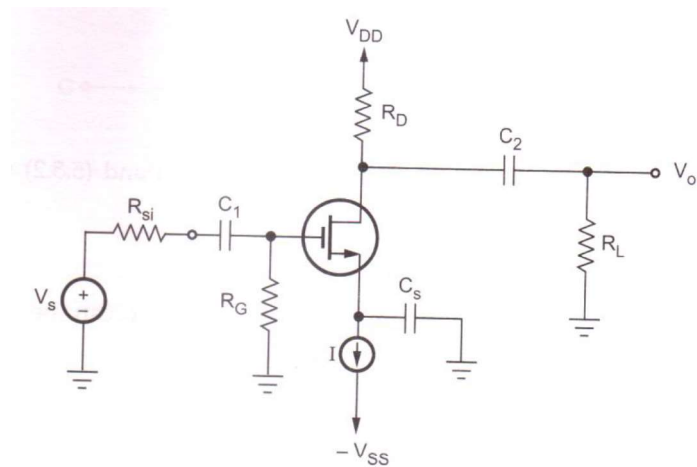


Fig 4.21. CS MOSFET amplifier

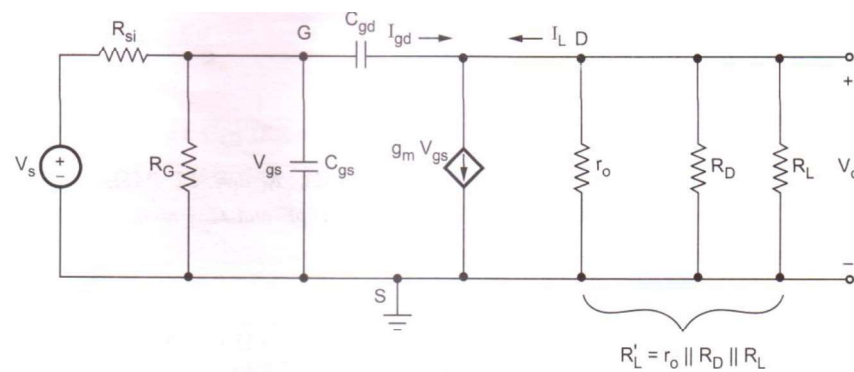


Fig 4.22. Equivalent circuit for CS MOSFET amplifier

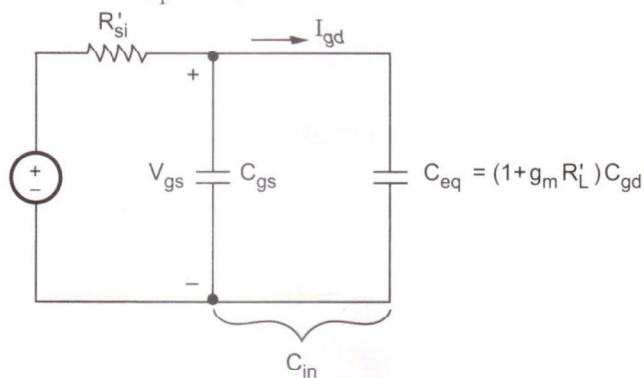


Fig 4.23. Input node

$$A_v = \frac{V_o}{V_i} = \frac{g_m V_{gs} R'_L}{V_{gs}} = g_m R'_L$$

$$C_{eq} = (1 + g_m R'_L)C_{gd}$$

The total capacitance  $C_{in}$ ,

$$\begin{aligned} C_{in} &= C_{gs} + C_{eq} \\ &= c_{gs} + (1 + g_m R'_L)C_{gd} \end{aligned}$$

The total resistance,


$$\begin{aligned} R_{si}' &= R_{si} || R_G \\ \tau &= RC = R_{si}' C_{in} \end{aligned}$$

$$\omega_H = \omega_o = \frac{1}{\tau}$$

$$= \frac{1}{R_{si}' C_{in}}$$

$$f_H = \frac{1}{2\pi R_{si}' C_{in}}$$

#### 4.10. Low frequency response:

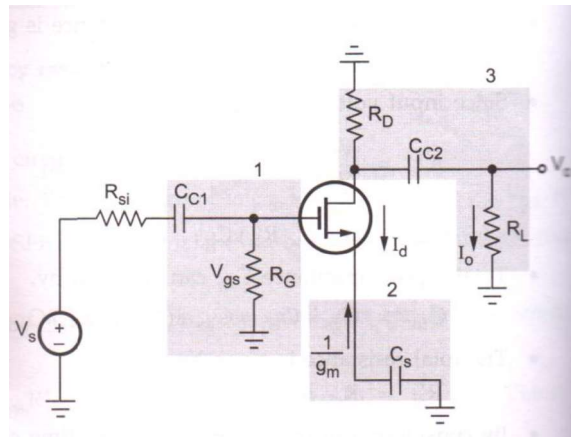

**Fig 4.24. Low frequency response of CS MOSFET amplifier circuit**

The corner frequencies due to there RC networks can be given by,

$$f_1 = \frac{1}{2\pi C_{c1} (R_{si} + R_G)}$$

$$f_1' = \frac{g_m}{2\pi C_s}$$

$$f_2'' = \frac{1}{(2\pi C_{c2} (R_D + R_L))}$$

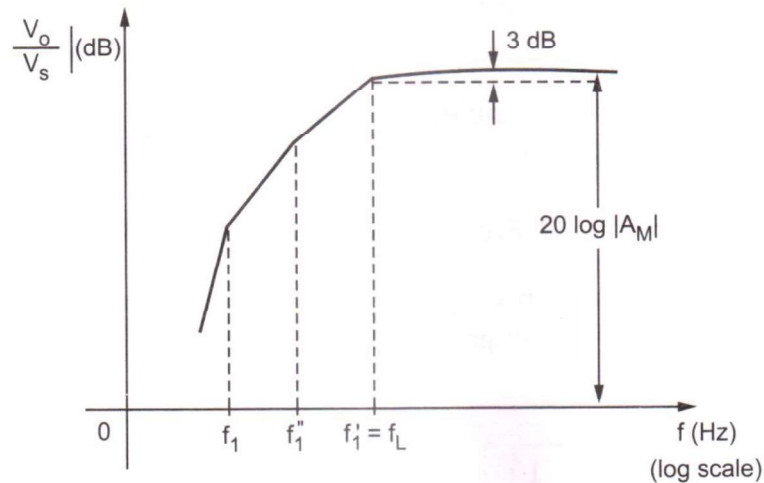


Fig 4.25. Low frequency response of CS MOSFET amplifier

#### 4.11. Bandwidth of Multistage Amplifier:

The Bandwidth of Multistage Amplifier is always less than that of the bandwidth of single stage amplifier.

##### 4.11.1. Overall lower cut off frequency of multistage amplifier:

Let us consider the lower 3db frequency of  $n$  identical cascaded stages as  $f_L(n)$ . It is the frequency for which the overall gain falls to  $\frac{1}{\sqrt{2}}$  (3dB) of its midband value.

$$\left[ \frac{1}{\sqrt{1 + \left( \frac{f_L}{f_L(n)} \right)^2}} \right]^n = \frac{1}{\sqrt{2}}$$

$$\sqrt{2} = \left[ \sqrt{1 + \left( \frac{f_L}{f_L(n)} \right)^2} \right]^n$$

Squaring on both sides,

$$2 = \left[ \sqrt{1 + \left( \frac{f_L}{f_{L(n)}} \right)^2} \right]^n$$

Taking  $n^{\text{th}}$  root on both sides,

$$2^{\frac{1}{n}} = 1 + \left( \frac{f_L}{f_{L(n)}} \right)^2$$

$$2^{\frac{1}{n}} - 1 = \left( \frac{f_L}{f_{L(n)}} \right)^2$$

Taking square root on both sides,

$$\sqrt{2^{\frac{1}{n}} - 1} = \frac{f_L}{f_{L(n)}}$$

$$f_{L(n)} = \frac{f_L}{\sqrt{2^{\frac{1}{n}} - 1}}$$

$$\sqrt{2^{\frac{1}{n}} - 1} = \frac{f_L}{f_{L(n)}}$$

$$f_{L(n)} = \frac{f_L}{\sqrt{2^{\frac{1}{n}} - 1}}$$

where  $f_{L(n)}$  – Lower 3dB frequency of identical cascaded stages.

$f_L$  –Lower 3dB frequency of single stage.

$n$  –Number of stages.

#### 4.11.2. Overall higher cut off frequency of multistage amplifier:

Let us consider the upper 3dB frequency of  $n$  identical stages as  $f_H(n)$ . It is the frequency for which the overall gain falls to  $\frac{1}{\sqrt{2}}$  (3dB) of its midband value.

$$\left[ \frac{1}{\sqrt{1 + \left( \frac{f_H(n)}{f_H} \right)^2}} \right]^n = \frac{1}{\sqrt{2}}$$

$$\sqrt{2} = \left[ \sqrt{1 + \left( \frac{f_H(n)}{f_H} \right)^2} \right]^n$$

Squaring on both sides,

$$2 = \left[ \sqrt{1 + \left( \frac{f_H(n)}{f_H} \right)^2} \right]^n$$

Taking  $n^{\text{th}}$  root on both sides,

$$2^{\frac{1}{n}} = 1 + \left( \frac{f_H(n)}{f_H} \right)^2$$

$$2^{\frac{1}{n}} - 1 = \left( \frac{f_H(n)}{f_H} \right)^2$$

Taking square root on both sides,

$$\sqrt{2^{\frac{1}{n}} - 1} = \frac{f_H(n)}{f_H}$$

$$f_{H(n)} = f_H \cdot \sqrt{2^{\frac{1}{n}} - 1}$$

In multistage amplifier  $f_{L(n)}$  is always greater than  $f_L$  and  $f_{H(n)}$  is always less than  $f_H$ . Therefore, we can say that bandwidth of multistage amplifier is always less than single stage amplifier.

If stages are not identical  $f_H$  can be given as,

$$\frac{1}{f_H} = 1.1 \sqrt{\sqrt{\frac{1}{f_1^2} + \frac{1}{f_2^2} + \frac{1}{f_3^2} + \dots + \frac{1}{f_n^2}}}$$



**SOLVED EXAMPLES:**

**1. For an amplifier, midband gain=100 and lower cut off frequency is 1KHz. Find the gain of an amplifier at frequency=20KHz.**

**Solution:** We know that, Bellow midband:

$$A = \frac{A_{mid}}{\sqrt{1 + (f/f_2)^2}}$$

$$A = \frac{100}{\sqrt{1 + \left(\frac{1000}{20}\right)^2}} = 2$$

**2. For an amplifier, 3db gain is 200 and higher cut off frequency is 20KHz. Find the gain of an amplifier at frequency=100KHz.**

**Solution :**

We know that,  $A_{mid} = 3\text{db gain} \times \sqrt{2} = 200 \times \sqrt{2} = 282.84$


Above midband:

$$A = \frac{A_{mid}}{\sqrt{1 + (f/f_2)^2}}$$

$$A = \frac{282.84}{\sqrt{1 + \left(\frac{100 \times 10^3}{20 \times 10^3}\right)^2}}$$

$$= 55.46$$

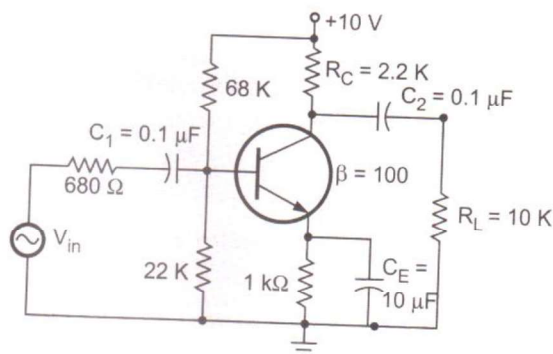**3. Determine the low frequency response of the amplifier circuit shown in fig.**



**Solution:** It is necessary to analyze each network to determine the critical frequency of the amplifier

a) Input RC network

$$f_c(\text{input}) = \frac{1}{2\pi[R_S + (R_1 \parallel R_2 \parallel h_{ie})]C_1}$$

$$= \frac{1}{2\pi[680 + (68K \parallel 22K \parallel 1.1K)]0.1 \times 10^{-6}}$$

$$= \frac{1}{2\pi[680 + 1031.7]0.1 \times 10^{-6}} = 929.8\text{Hz}$$

b) Output RC network

$$f_c(\text{output}) = \frac{1}{2\pi(R_C + R_L)C_2} = \frac{1}{2\pi(2.2K + 10K)0.1 \times 10^{-6}} = 130.45\text{Hz}$$


c) Bypass RC network

$$f_c(\text{bypass}) = \frac{1}{2\pi\left[\left(\frac{R_{TH} + h_{ie}}{\beta}\right) \parallel R_E\right]C_E}$$

$$R_{TH} = R_1 \parallel R_2 \parallel R_S = 68K \parallel 22K \parallel 680 = 653.28\Omega$$


$$f_c(\text{bypass}) = \frac{1}{2\pi\left[\left(\frac{653.28 + 1100}{100}\right) \parallel 1K\right]10 \times 10^{-6}} = \frac{1}{2\pi[17.23]10 \times 10^{-6}}$$

$$= 923.7\text{Hz}$$

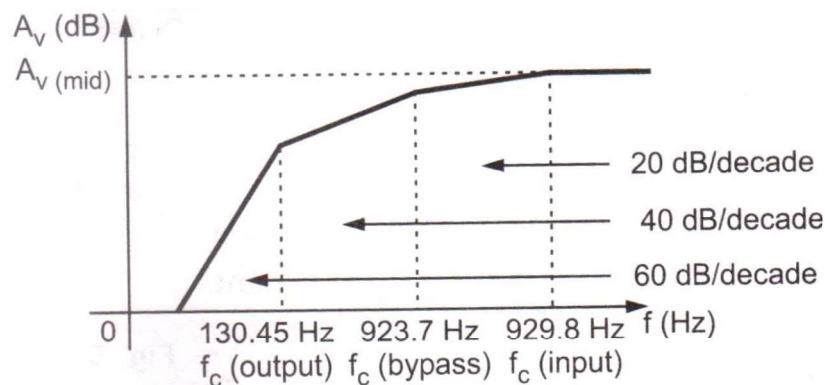

4. Calculate the cut off frequency due to  $C_1$  and  $C_2$  in the circuit shown in fig.

1)  $h_{fe}=300$       2)  $h_{ie}=32k$

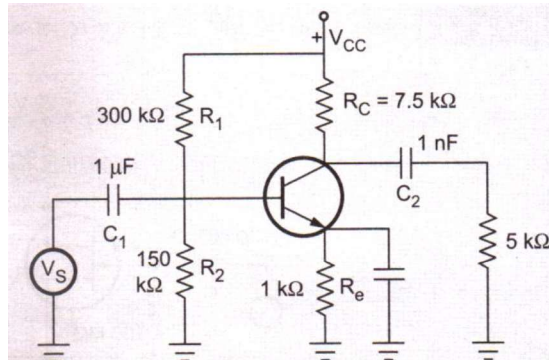

**Solution:**

1) cut off frequency due to  $C_1$

$$f_c = \frac{1}{2\pi R_{in} C_1} \quad R_{in} = R_1 \parallel R_2 \parallel h_{ie}$$


$$= \frac{1}{2\pi [(R_1 \parallel R_2 \parallel h_{ie})] C_1}$$

$$= \frac{1}{2\pi [(300 \times 10^3 \parallel 150 \times 10^3 \parallel 32 \times 10^3)] (1 \times 10^{-6})} = 6.565 \text{ Hz}$$

2) cut off frequency due to  $C_2$

$$f_c = \frac{1}{2\pi (R_C + R_L) C_2} = \frac{1}{2\pi (7.5 \times 10^3 + 5 \times 10^3) 0.1 \times 10^{-9}} = 12732.4 \text{ Hz}$$

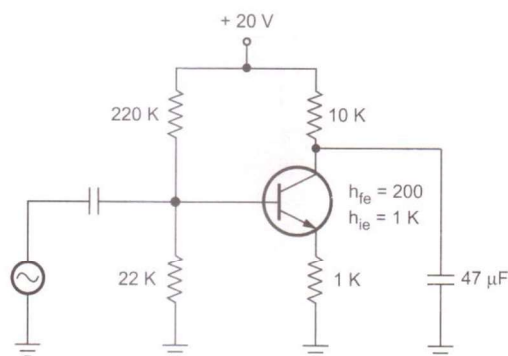5. Determine the cut off frequency due to the bypass capacitor in the fig.



**Solution:**

$$f_{C(\text{bypass})} = \frac{1}{2\pi \left[ \left( \frac{R_{TH} + h_{ie}}{\beta} \right) \parallel R_E \right] C_E}$$

$$R_{TH} = R_1 \parallel R_2 \parallel R_S = 220K \parallel 22K \parallel 0 = 0$$

$$f_{C(\text{bypass})} = \frac{1}{2\pi \left[ \left( \frac{1000}{200} \right) \parallel 1 \times 10^3 \right] 47 \times 10^{-6}} = \frac{1}{2\pi [4.97] 47 \times 10^{-6}} = 681\text{Hz}$$

**6. At  $I_C=1\text{mA}$  and  $V_{CE}=10\text{V}$ , a certain transistor data shows  $C_\mu=C_\mu=3\text{pF}$   $h_{fe}=200$  and  $\omega_T=500\text{M rad/sec}$ . Calculate  $g_m, r_\pi, C_\pi=C_\pi$  and  $\omega_\beta$**

**Solution:**

$$\text{i) } g_m = \frac{I_C}{V_T} = \frac{1\text{mA}}{26\text{mV}} = 38.46\text{mA/V}$$

$$\text{ii) } r_\pi = \frac{h_{fe}}{g_m} = \frac{200}{38.46 \times 10^3} = 5.20\text{K}\Omega$$

$$\text{iii) } (C_\pi + C_\mu) = \frac{g_m}{2\pi f_T} = \frac{g_m}{\omega_T} = \frac{38.46 \times 10^{-3}}{500 \times 10^6}$$

$$(C_\pi + C_\mu) = 76.92\text{pF}$$

$$C_\pi = C_\pi = 76.92\text{pF} - 3\text{pF} = 73.92\text{pF}$$

iv) We know that,

$$f_T = h_{fe} f_\beta$$

$$2\pi f_T = 2\pi h_{fe} f_\beta$$

$$\omega_T = h_{fe} \omega_\beta$$

$$\omega_\beta = \frac{\omega_T}{h_{fe}} = 2.5\text{M} \frac{\text{rad}}{\text{sec}}$$

**7. Short circuit CE current gain of transistor is 25 at a frequency of 2MHz if  $f_\beta=200\text{KHz}$  calculate 1) $f_T$  2) $h_{fe}$  3) find  $|A_i|$  at frequency of 10MHz and 100MHz.**

**Solution:**

$$\begin{aligned} \text{i) } f_T &= |A_i| \times f = 25 \times 2 \times 10^6 \\ &= 50\text{MHz} \end{aligned}$$

$$\text{ii) } h_{fe} = \frac{f_T}{f_\beta} = \frac{50\text{MHz}}{200\text{KHz}} = 250\text{KHz}$$

$$\text{iii) } |A_i| = \frac{h_{fe}}{\sqrt{1 + \left(\frac{f}{f_\beta}\right)^2}}$$

At  $f = 10\text{MHz}$

$$|A_i| = \frac{250}{\sqrt{1 + \left(\frac{10 \times 10^6}{200 \times 10^3}\right)^2}} = 5$$

At  $f = 100\text{MHz}$

$$|A_i| = \frac{250}{1 + \left(\frac{100 \times 10^6}{200 \times 10^3}\right)^2} = 0.5$$

**8. A high frequency amplifier uses a transistor which is driven from a source with  $R_s=0$ . Calculate value of  $f_H$ , if  $R_L=0$  and  $R_L=1\text{K}\Omega$ . Assume typical values of hybrid- $\pi$  parameters.**

**Solution:**

**1)  $f_H$**

**For  $R_L=0$**

$$f_H = \frac{1}{2\pi r_\pi [C_\pi + C_\mu]}$$

Typical values:  $r_\pi = 1\text{k}$ ,  $C_\pi = 100\text{pF}$ ,  $C_\mu = 3\text{pF}$

$$f_H = \frac{1}{2\pi \times 1 \times 10^3 (100 \times 10^{-12} + 3 \times 10^{-12})} = 1.545\text{MHz}$$

**For  $R_L=1\text{K}$**


$$f_H = \frac{1}{2\pi r_\pi [C_\pi + C_\mu (1 + g_m R_L)]}$$

Typical values:  $r_\pi = 1\text{k}$ ,  $C_\pi = 100\text{pF}$ ,  $C_\mu = 3\text{pF}$ ,  $g_m = 50\text{mA/V}$

$$f_H = \frac{1}{2\pi \times 1 \times 10^3 [100 \times 10^{-12} + 3 \times 10^{-12} (1 + 50 \times 10^{-3} \times 1 \times 10^3)]}$$

$$= 0.629 \text{ MHz}$$

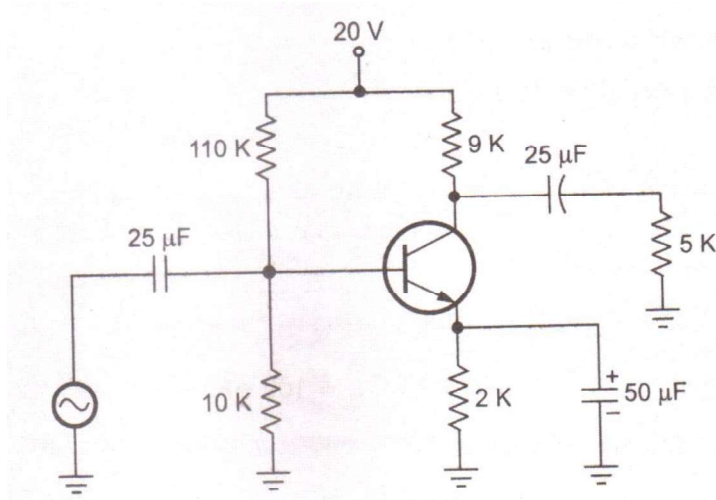9. Determine the bandwidth of the amplifier shown.



$$r_b = 100\Omega, r_{\pi} = 1.1\text{K}, C_{\pi} = 3\text{pF}, C_{\mu} = 100\text{pF}, h_{fe} = 225$$

**Solution:**

We know that,

$$h_{fe} = r_b + r_{\pi} = 100\Omega + 1.1\text{k} = 1.2\text{k}$$

$$f_{c(\text{input})} = \frac{1}{2\pi [R_S + (R_1 \parallel R_2 \parallel h_{ie})] C_1}$$

$$= \frac{1}{2\pi [0 + (110\text{K} \parallel 10\text{K} \parallel 1.2\text{K})] 25 \times 10^{-6}} = 6\text{Hz}$$

$$f_{c(\text{output})} = \frac{1}{2\pi (R_C + R_L) C_2} = \frac{1}{2\pi (9\text{K} + 5\text{k}) 25 \times 10^{-6}} = 0.454\text{Hz}$$

$$f_{c(\text{bypass})} = \frac{1}{2\pi \left[ \left( \frac{R_{TH} + h_{ie}}{\beta} \right) \parallel R_E \right] C_E}$$

$$R_{TH} = R_1 \parallel R_2 \parallel R_S = 110\text{K} \parallel 10\text{K} \parallel 0 = 0\Omega$$

$$f_{C(\text{bypass})} = \frac{1}{2\pi \left[ \left( \frac{1.2 \times 10^3}{225} \right) \parallel 2 \times 10^3 \right] 50 \times 10^{-6}} = 598 \text{Hz}$$

$f_L$  is the smallest of the three i. e. 0.454Hz

$$f_H = \frac{1}{2\pi r_{\pi} [C_{\pi} + C_{\mu}(1 + g_m R_L)]}$$

$$C_{\pi} = 3 \text{pF}, C_{\mu} = 100 \text{pF}$$

$$g_m = \frac{h_{fe}}{r_{\pi}} = \frac{225}{1.1 \times 10^3} = 204.5 \text{mA/V}$$

$$f_H = \frac{1}{2\pi \times 1.1 \times 10^3 [3 \times 10^{-12} + 100 \times 10^{-12} (1 + 204.5 \times 10^{-3} \times 5 \times 10^3)]}$$

$$= 1.4136 \text{KHz}$$

$$\text{Bandwidth} = f_H - f_L = 1.4136 \times 10^3 - 0.454 = 1.4131 \text{ KHz}$$

**10. For n-channel MOSFET,  $L=1.0\mu\text{m}$ ,  $L_{ov}=0.05\mu\text{m}$ ,  $W=10\mu\text{m}$ ,  $C_{ox}=3.45 \times 10^{-3} \text{F/m}^2$ ,  $I_D=200\mu\text{A}$  and  $K_n'=150\mu\text{A/V}^2$ . Find the  $f_T$  if MOSFET is operating in the triode region.**

**Solution:**

$$C_{ox} = 3.45 \times 10^{-3} \text{F/m}^2 = 3.45 \times 10^{-15} \text{F}/\mu\text{m}^2$$

$$C_{gd} = C_{gs} = \frac{1}{2} W L C_{ox} + C_{ov} = \frac{1}{2} W L C_{ox} + W L_{ov} C_{ox}$$

$$= \left( \frac{1}{2} \times 10 \times 1 \times 3.45 \times 10^{-15} \right) + 10 \times 0.05 \times 3.45 \times 10^{-15}$$

$$= 17.25 \times 10^{-15} + 1.725 \times 10^{-15} = 18.975 \times 10^{-15} \text{F}$$

$$= 18.975 \text{fF}$$

$$g_m = \sqrt{2K_n'} \sqrt{W/L} \sqrt{I_D}$$

$$= \sqrt{2 \times 150 \times 10^{-6}} \sqrt{10/1} \sqrt{200 \times 10^{-6}} = 0.7746 \text{ mA/V}$$

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})} = \frac{0.7746 \times 10^{-3}}{2\pi \times (18.975 + 18.975) \times 10^{-15}} = 3.2485 \text{GHz}$$

**11. For CS MOSFET amplifier,  $R_{si}=120k\Omega$ ,  $R_G=4.7M\Omega$ ,  $R_D=10K$ ,  $R_L=15K$ ,  $g_m=1.2mA/V$ ,  $r_o=150K\Omega$ ,  $C_{gs}=0.3pF$ . Find the midband gain  $A_M$  and the upper 3dB frequency,  $f_H$ .**

**Solution:**

$$A_M = -\frac{R_G}{R_G + R_{si}} g_m R'_L$$

$$\text{where } R'_L = r_o \parallel R_D \parallel R_L = 150K \parallel 10K \parallel 15K = 5.77K\Omega$$

$$A_M = -\frac{4.7 \times 10^6}{4.7 \times 10^6 + 120 \times 10^3} \times 1.2 \times 10^{-3} \times 5.77 \times 10^3$$

$$= -6.75$$

$$C_{eq} = (1 + g_m R'_L) C_{gd}$$

$$= (1 + 1.2 \times 10^{-3} \times 5.77 \times 10^3) \times 0.3 \times 10^{-12} = 2.377pF$$

$$C_{in} = C_{eq} + C_{gs} = 2.377 + 1 = 3.377pF$$

$$f_H = \frac{1}{2\pi R'_{si} C_{in}} \quad \text{where } R'_{si} = R_{si} \parallel R_G = 120K \parallel 4.7M = 117K$$

$$= \frac{1}{2\pi \times 117 \times 10^3 \times 3.377 \times 10^{-12}} = 402.8KHz$$

**12. For a CS MOSFET amplifier,  $C_{C1}=C_S=C_{C2}=1\mu F$ ,  $R_G=12M\Omega$ ,  $R_{si}=180K\Omega$ ,  $g_m=1.2mA/V$ ,  $R_D=10K$  and  $R_L=15K$ . Calculate  $A_M$ ,  $f_1$ ,  $f_1'$ ,  $f_1''$  and  $f_L$ .**

**Solution:**

$$A_M = -\left(\frac{R_G}{R_G + R_{si}}\right) g_m (R_D \parallel R_L) \quad \text{where } R_D \parallel R_L = 10K \parallel 15K = 6K$$

$$= -\left(\frac{12M}{12M + 180K}\right) 1.2 \times 6 = -7.09$$

$$f_1 = \frac{1}{2\pi \times 1 \times 10^{-6} (180 \times 10^3 + 12 \times 10^6)} = 0.013Hz$$

$$f_1' = \frac{g_m}{2\pi C_S} = \frac{1.2 \times 10^{-3}}{2\pi \times 1 \times 10^{-6}} = 190.98Hz$$

$$f_1'' = \frac{1}{2\pi \times C_{C2} (R_D + R_L)} = \frac{1}{2\pi \times 1 \times 10^{-6} (25 \times 10^3)} = 6.366Hz$$



Here,  $f_1'' > f_1$  and hence

$$f_L = f_1' = 190.98\text{Hz}$$

## TWO MARK QUESTIONS AND ANSWERS

### 1. What is roll off?

The frequency response is nearly ideal over a wide range of mid frequency. Only at low and high frequency ends, gain deviates from ideal characteristics. The decrease in voltage gain with frequency is called as roll off.

### 2. What is bandwidth of an amplifier?

Bandwidth of the amplifier is defined as the difference between upper cut-off and lower cut-off frequencies.

$$\text{Bandwidth} = f_2 - f_1$$

The frequency  $f_2$  lies in high frequency region while the frequency  $f_1$  lies in low frequency region.

### 3. What is the significance of octaves and decades in frequency response?

The octaves and decades are the measures of change in frequency. A ten times change in frequency is called a decade. On the other hand, octave corresponds to doubling or halving of the frequency. For example, increase in frequency from 100Hz to 200Hz is an octave. Likewise, a decrease in frequency from 100 kHz to 50kHz is also an octave.

### 4. State Miller theorem using resistor and capacitor.

For the analysis purpose, in transistor amplifiers, it is necessary to split the capacitance between input(base or gate) and the output(collector or drain). The capacitance may be  $C_{bc}$  (in case of BJT) or  $C_{gd}$  (in case of FET). This can be achieved using Miller's theorem.

Miller's theorem: i) For resistor-  $\frac{Z}{1-K}$ ,  $\frac{ZK}{K-1}$

ii) For capacitor-  $C(A_v + 1)$ ,  $C\left(\frac{A_v + 1}{A_v}\right)$

### 5. Derive the expression for midband gain.

In the midband, the voltage gain of the amplifier is approximately maximum. It is designated as midband gain or  $A_{mid}$ .

$$A = \frac{A_{mid}}{\sqrt{1 + (f_1/f)^2} \sqrt{1 + (f/f_2)^2}}$$