



Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code : 50440

B.E./B.Tech. DEGREE EXAMINATION, NOVEMBER/DECEMBER 2017
Fourth Semester
Electronics and Communication Engineering
EC 6404 – LINEAR INTEGRATED CIRCUITS
(Common to Medical Electronics/Robotics and Automation Engineering)
(Regulations 2013)

Time : Three Hours

Maximum : 100 Marks

Answer ALL questions

PART – A

(10×2=20 Marks)

1. Draw the dc transfer characteristics of a BJT differential amplifier and define differential mode input voltages.
2. The power supply rejection of an op-amp is 80dB for a 1V change in supply voltage. Calculate the change in offset voltage.
3. State the limitations of an ideal integrator.
4. How will you realize a peak detector using a precision rectifier ?
5. Mention the need of pre-distortion circuits in Gilbert analog multiplier and how is the configuration of Gilbert multiplier done with pre-distortion circuits.
6. Define capture-range and lock-range of PLL.
7. How is the classification of A/D converters carried out based on their operational features ?
8. Find the number of resistors required for an 8-bit weighted resistor D/A converter. Consider the smallest resistance is R and obtain those resistance values.
9. Define current transfer ratio of an opto-coupler.
10. Draw a fixed voltage regulator circuit and state its operations.

50440

-2-



PART - B

(5×13=65 Marks)

11. a) i) With a help of a block diagram, explain the various stages present in an operational amplifier. (6)
ii) Draw the transfer characteristics of an operational amplifier and explain the linear and non-linear operation. (7)
(OR)
- b) i) Draw the inverting and non-inverting amplifier circuits of an op-amp in closed-loop configuration. Obtain the expressions for the closed-loop gain in these circuits. (8)
ii) Perform the AC analysis of the operational amplifier 741. (5)
12. a) i) For performing differentiation in an operational amplifier, integrator is preferred to differentiator – Explain. (6)
ii) What is an instrumentation amplifier ? Draw a system whose gain is controlled by a variable resistance. (7)
(OR)
- b) i) Design a clipper circuit for a clipping level of +0.61V, given an input sine wave signal of 0.5V peak. Assume the gain of the amplifier is 12 and it has an input resistance of 1k-ohm connected. (7)
ii) Design a second order Butterworth low-pass filter having upper cut-off frequency of 2.5 kHz. (6)
13. a) i) Write notes on basic analog multiplication techniques. (5)
ii) Explain the operation of a variable transconductance multiplier circuit. Derive the expression for its output voltage. (8)
(OR)
- b) i) Derive the expression for free running frequency of voltage controlled oscillator. (5)
ii) Explain the process of FSK demodulation using PLL. How is the stability of the frequency obtained in a PLL by the use of voltage controlled oscillator ? (8)
14. a) i) Explain in detail on the operational features of 4-bit weighted resistor type D/A converter. (7)
ii) Differentiate between current mode and voltage mode R-2R ladder D/A converters. (6)

(OR)



- b) i) With a neat block diagram, explain the operation of successive approximation type A/D converter in detail. (5)
- ii) An 8-bit A/D converter accepts an input voltage signal of range 0 to 9V. What is the minimum value of the input voltage required for generating a change of 1 least significant bit? Specify the digital output for an input voltage of 4 V. What input voltage will generate all 1s at the A/D converter output? (8)
15. a) i) With neat diagram, explain the operation of an astable and monostable multivibrators. (8)
- ii) Draw the functional diagram and connection diagram of a low voltage regulator and explain. (5)
- (OR)
- b) i) Draw the block diagram of a typical IC audio power amplifier and briefly explain their salient features. (6)
- ii) Design a frequency to voltage converter using IC VFC 32 for a full scale output of 8 V for a full scale input frequency of 80 kHz with a maximum ripple of 8 mV. (7)

PART - C

(1×15=15 Marks)

16. a) i) Design a differentiator to produce an output of 4 V when the input changes by 2 V in 60 micro seconds. (5)
- ii) A PLL has a free running frequency of 400 kHz and the band-width of the low pass filter is 8 kHz. Will the loop tend to acquire lock for an input signal of 550 kHz? Explain. In this case, assume that the phase detector produces sum and difference frequency components. (10)
- (OR)
- b) i) Design a square wave generator using 555 timer for a frequency of 120 Hz and 60% duty cycle. Assume $C = 0.2 \mu F$. (7)
- ii) For a 4-bit R-2R ladder D/A converter assume that the full scale voltage is 12 V. Calculate the step change in output voltage on input varying from 1001 to 1111. (8)



- b) i) With a neat block diagram, explain the operation of successive approximation type A/D converter in detail. (5)
- ii) An 8-bit A/D converter accepts an input voltage signal of range 0 to 9V. What is the minimum value of the input voltage required for generating a change of 1 least significant bit? Specify the digital output for an input voltage of 4 V. What input voltage will generate all 1s at the A/D converter output? (8)
15. a) i) With neat diagram, explain the operation of an astable and monostable multivibrators. (8)
- ii) Draw the functional diagram and connection diagram of a low voltage regulator and explain. (5)
- (OR)
- b) i) Draw the block diagram of a typical IC audio power amplifier and briefly explain their salient features. (6)
- ii) Design a frequency to voltage converter using IC VFC 32 for a full scale output of 8 V for a full scale input frequency of 80 kHz with a maximum ripple of 8 mV. (7)

PART - C

(1×15=15 Marks)

16. a) i) Design a differentiator to produce an output of 4 V when the input changes by 2 V in 60 micro seconds. (5)
- ii) A PLL has a free running frequency of 400 kHz and the band-width of the low pass filter is 8 kHz. Will the loop tend to acquire lock for an input signal of 550 kHz? Explain. In this case, assume that the phase detector produces sum and difference frequency components. (10)
- (OR)
- b) i) Design a square wave generator using 555 timer for a frequency of 120 Hz and 60% duty cycle. Assume $C = 0.2 \mu\text{F}$. (7)
- ii) For a 4-bit R-2R ladder D/A converter assume that the full scale voltage is 12 V. Calculate the step change in output voltage on input varying from 1001 to 1111. (8)