

4.3 Intel 8253/54 - Programmable Interval Timer

The Intel 8253 and 8254 are Programmable Interval Timers (PTIs) designed for microprocessors to perform timing and counting functions using three 16-bit registers. Each counter has 2 input pins, i.e. Clock & Gate, and 1 pin for “OUT” output. To operate a counter, a 16-bit count is loaded in its register. On command, it begins to decrement the count until it reaches 0, then it generates a pulse that can be used to interrupt the CPU. The following table differentiates the features of 8253 and 8254,

8253	8254
Its operating frequency is 0 - 2.6 MHz	Its operating frequency is 0 - 10 MHz
It uses N-MOS technology	It uses H-MOS technology
Read-Back command is not available	Read-Back command is available
Reads and writes of the same counter cannot be interleaved.	Reads and writes of the same counter can be interleaved.

The most prominent features of 8253/54 are as follows –

- It has three independent 16-bit down counters.
- It can handle inputs from DC to 10MHz.
- These three counters can be programmed for either binary or BCD count.
- It is compatible with almost all microprocessors.
- 8254 has a powerful command called READ BACK command, which allows the user to check the count value, the programmed mode, the current mode, and the status of the counter.

8254 Architecture:

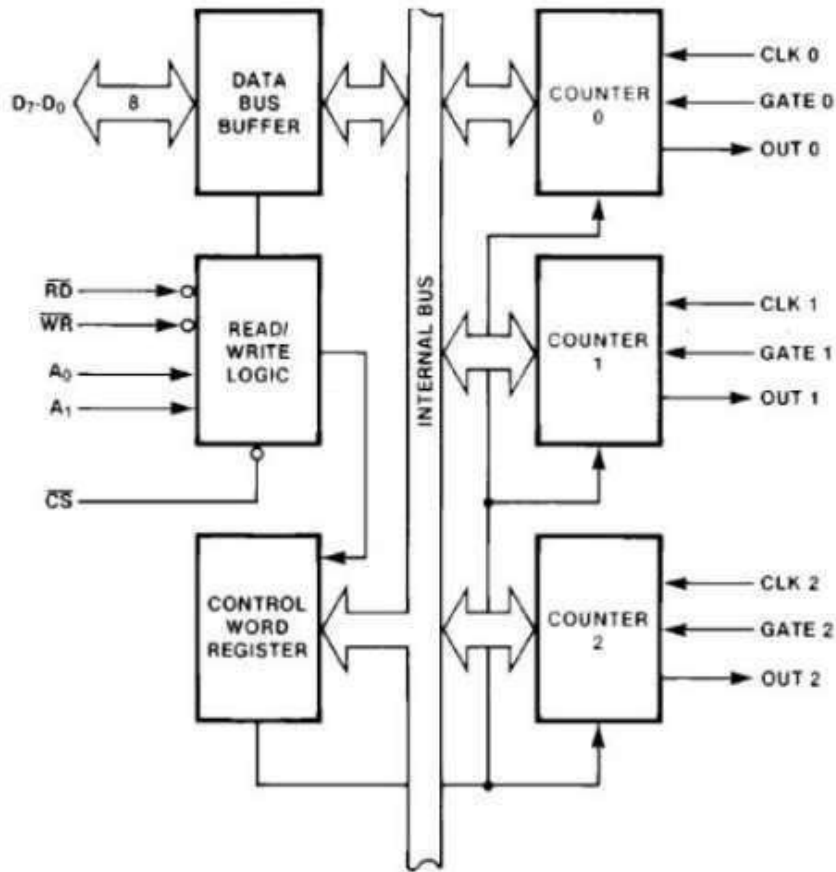


Figure 4.2.2 Architecture of 8254

[Source: "Microprocessor Architecture Programming and Application" by R.S. Gaonkar, page-]

8254 Pin Description

 


Figure 4.2.3 Pin diagram of 8254

[Source: "Microprocessor Architecture Programming and Application" by R.S. Gaonkar, page-]

In the above figure, there are three counters, a data bus buffer, Read/Write control logic, and a control register. Each counter has two input signals - CLOCK & GATE, and one output signal - OUT.

Data Bus Buffer

It is a tristate, bi-directional, 8-bit buffer, which is used to interface the 8253/54 to the system data bus. It has three basic functions –

- Programming the modes of 8253/54.
- Loading the count registers.
- Reading the count values.

Read/Write Logic

It includes 5 signals, i.e. RD, WR, CS, and the address lines A0 & A1. In the peripheral I/O mode, the RD and WR signals are connected to IOR and IOW, respectively. In the memory mapped I/O mode, these are connected to MEMR and MEMW. Address lines A0 & A1 of the CPU are connected to lines A0 and A1 of the 8253/54, and CS is tied to a decoded address. The control word register and counters are selected according to the signals on lines A0 & A1.

A ₁	A ₀	Result
0	0	Counter 0
0	1	Counter 1
1	0	Counter 2
1	1	Control Word Register
X	X	No Selection

Control Word Register


This register is accessed when lines A0 & A1 are at logic 1. It is used to write a command word, which specifies the counter to be used, its mode, and either a read or write operation. Following table shows the result for various control inputs.

A ₁	A ₀	RD	WR	CS	Result
0	0	1	0	0	Write Counter 0
0	1	1	0	0	Write Counter 1
1	0	1	0	0	Write Counter 2
1	1	1	0	0	Write Control Word
0	0	0	1	0	Read Counter 0
0	1	0	1	0	Read Counter 1
1	0	0	1	0	Read Counter 2
1	1	0	1	0	No operation
X	X	1	1	0	No operation
X	X	X	X	1	No operation

Counters

Each counter consists of a single, 16 bit-down counter, which can be operated in either binary or BCD. Its input and output is configured by the selection of modes stored in the control word register. The programmer can read the contents of any of the three counters without disturbing the actual count in process.

Control Word Format

 

SC—Select Counter

SC1	SC0	
0	0	Select Counter 0
0	1	Select Counter 1
1	0	Select Counter 2
1	1	Read-Back Command (see Read Operations)

M—Mode

M2	M1	M0	
0	0	0	Mode 0
0	0	1	Mode 1
X	1	0	Mode 2
X	1	1	Mode 3
1	0	0	Mode 4
1	0	1	Mode 5

RW—Read/Write

RW1	RW0	
0	0	Counter Latch Command (see Read Operations)
0	1	Read/Write least significant byte only
1	0	Read/Write most significant byte only
1	1	Read/Write least significant byte first, then most significant byte

BCD

0	Binary Counter 16-bits
1	Binary Coded Decimal (BCD) Counter (4 Decades)

Figure 4.2.3 Control word of 8254

[Source: "Microprocessor Architecture Programming and Application" by R.S. Gaonkar, page-]

Intel 8253/54 - Operational Modes

8253/54 can be operated in 6 different modes. In this chapter, we will discuss these operational modes.

Mode 0 – Interrupt on Terminal Count

- It is used to generate an interrupt to the microprocessor after a certain interval.
- Initially the output is low after the mode is set. The output remains LOW after the count value is loaded into the counter.
- The process of decrementing the counter continues till the terminal count is reached, i.e., the count become zero and the output goes HIGH and will remain high until it reloads a new count.
- The GATE signal is high for normal counting. When GATE goes low, counting is terminated and the current count is latched till the GATE goes high again.

Mode 1 – Programmable One Shot

- It can be used as a mono stable multi-vibrator.
- The gate input is used as a trigger input in this mode.
- The output remains high until the count is loaded and a trigger is applied.

Mode 2 – Rate Generator

- The output is normally high after initialization.
- Whenever the count becomes zero, another low pulse is generated at the output and the counter will be reloaded.

Mode 3 – Square Wave Generator

- This mode is similar to Mode 2 except the output remains low for half of the timer period and high for the other half of the period.

Mode 4 – Software Triggered Mode

- In this mode, the output will remain high until the timer has counted to zero, at which point the output will pulse low and then go high again.
- The count is latched when the GATE signal goes LOW.
- On the terminal count, the output goes low for one clock cycle then goes HIGH. This low pulse can be used as a strobe.

Mode 5 – Hardware Triggered Mode

- This mode generates a strobe in response to an externally generated signal.
- This mode is similar to mode 4 except that the counting is initiated by a signal at the gate input, which means it is hardware triggered instead of software triggered.
- After it is initialized, the output goes high.
- When the terminal count is reached, the output goes low for one clock cycle.

4.1 8255-Program Peripheral Interface (Programmable Peripheral input-output port)

The parallel input-output port chip 8255 is also called as programmable peripheral input-output port. The Intel's 8255 are designed for use with Intel's 8-bit, 16-bit and higher capability microprocessors. It has 24 input/output lines which may be individually programmed in two groups of twelve lines each, or three groups of eight lines.

The two groups of I/O pins are named as Group A and Group B. Each of these two groups contains a subgroup of eight I/O lines called as 8-bit port and another subgroup of four lines or a 4-bit port. Thus Group A contains an 8-bit port A along with a 4-bit port C upper. Thus Group B contains an 8-bit port B along with a 4-bit port C lower.

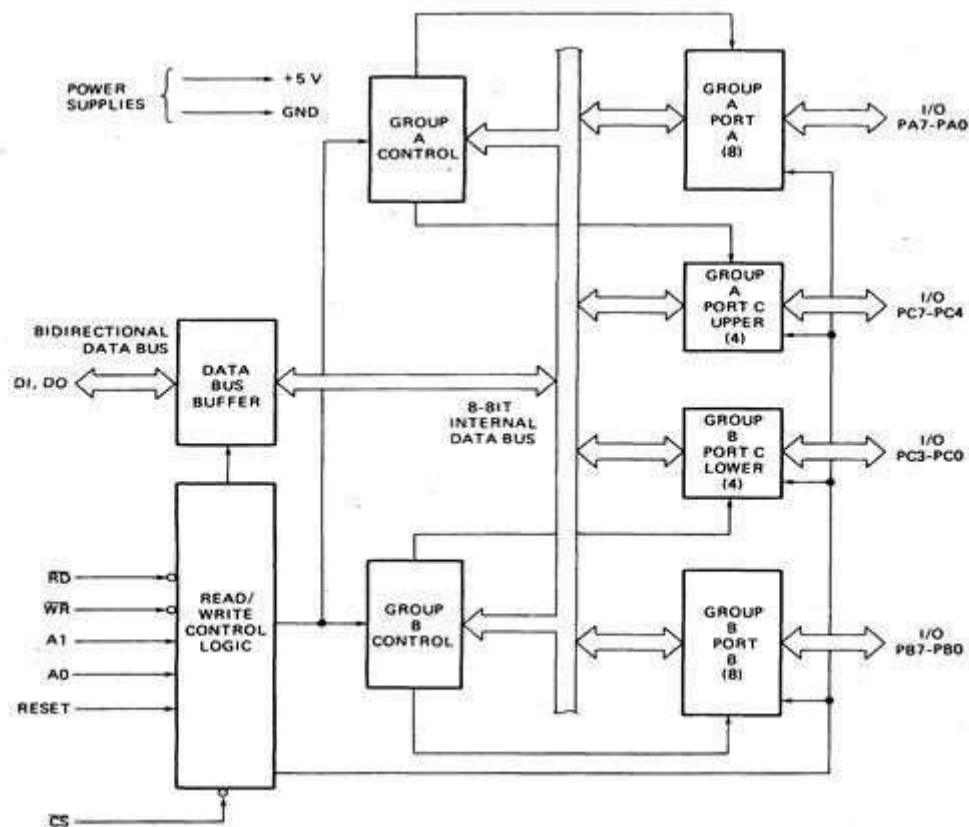


FIGURE Internal block diagram of 8255A programmable parallel port device. (Intel Corporation)

Figure 4.1.1 Architecture

[Source: "Microprocessor Architecture Programming and Application" by R.S. Gaonkar, page-]

The port A lines are identified by symbols PA0-PA7 while the port C lines are identified as PC4-PC7 similarly. Group B contains an 8-bit port B, containing lines PB0-PB7 and a 4-bit port C with lower bits PC0-PC3. The port C upper and port C lower can be used in combination as an 8-bit port C. Both the port Cs is assigned the same address.

Thus one may have either three 8-bit I/O ports or two 8-bit and two 4-bit I/O ports from 8255. All of these ports can function independently either as input or as output ports. This can be achieved by programming the bits of an internal register of 8255 called as control word register (CWR). The internal block diagram and the pin configuration of 8255 are shown in figure 4.1.1.

The 8-bit data bus buffer is controlled by the read/write control logic. The read/write control logic manages all of the internal and external transfer of both data and control words. RD, WR, A1, A0 and RESET are the inputs, provided by the microprocessor to READ/WRITE control logic of 8255. The 8-bit, 3-state bidirectional buffer is used to interface the 8255 internal data bus with the external system data bus. This buffer receives or transmits data upon the execution of input or output instructions by the microprocessor. The control words or status information is also transferred through the buffer.

 


Figure 4.1.2 Pin Diagram of 8255A

[Source: "Microprocessor Architecture Programming and Application" by R.S. Gaonkar, page-]

- The port A lines are identified by symbols PA0-PA7 while the port C lines are identified as PC4-PC7. Similarly, Group B contains an 8-bit port B, containing lines PB0-PB7 and a 4-bit port C with lower bits PC0- PC3. The port C upper and port C lower can be used in combination as an 8-bit port C.
- Both the port C is assigned the same address. Thus one may have either three 8-bit I/O ports or two 8-bit and two 4-bit ports from 8255. All of these ports can function independently either as input or as output ports. This can be achieved by programming the bits of an internal register of 8255 called as control word register (CWR).
- The 8-bit data bus buffer is controlled by the read/write control logic. The read/write control logic manages all of the internal and external transfers of both data and control words.
- RD, WR, A1, A0 and RESET are the inputs provided by the microprocessor to the READ/ WRITE control logic of 8255. The 8-bit, 3-state bidirectional buffer is used to interface the 8255 internal data bus with the external system data bus.
- This buffer receives or transmits data upon the execution of input or output instructions by the microprocessor. The control words or status information is also transferred through the buffer.
- PA7-PA0: These are eight port A lines that acts as either latched output or buffered input lines depending upon the control word loaded into the control word register.
- PC7-PC4: Upper nibble of port C lines. They may act as either output latches or input buffers lines.
- This port also can be used for generation of handshake lines in mode1 or mode2.
- PC3-PC0: These are the lower port C lines; other details are the same as PC7- PC4 lines.
- PB0-PB7: These are the eight port B lines which are used as latched output lines or buffered input lines in the same way as port A.
- RD: This is the input line driven by the microprocessor and should be low to indicate read operation to 8255.

- WR: This is an input line driven by the microprocessor. A low on this line indicates write operation.
- CS: This is a chip select line. If this line goes low, it enables the 8255 to respond to RD and WR signals, otherwise RD and WR signal are neglected.
- D0-D7: These are the data bus lines those carry data or control word to/from the microprocessor.
- RESET: Logic high on this line clears the control word register of 8255. All ports are set as input ports by default after reset.
- A1-A0: These are the address input lines and are driven by the microprocessor.
- These lines A1-A0 with RD, WR and CS from the following operations for 8255. These address lines are used for addressing any one of the four registers, i.e. three ports and a control word register as given in table below.

\overline{RD}	\overline{WR}	\overline{CS}	A ₁	A ₀	Input (Read) cycle
0	1	0	0	0	Port A to Data bus
0	1	0	0	1	Port B to Data bus
0	1	0	1	0	Port C to Data bus
0	1	0	1	1	CWR to Data bus

\overline{RD}	\overline{WR}	\overline{CS}	A ₁	A ₀	Output (Write) cycle
1	0	0	0	0	Data bus to Port A
1	0	0	0	1	Data bus to Port B
1	0	0	1	0	Data bus to Port C
1	0	0	1	1	Data bus to CWR

\overline{RD}	\overline{WR}	\overline{CS}	A ₁	A ₀	Function
X	X	1	X	X	Data bus tristated
1	1	0	X	X	Data bus tristated

Control Word Register

Figure 4.1.3 Control word Register of 8255A

[Source: "Microprocessor Architecture Programming and Application" by R.S. Gaonkar, page-]

Modes of Operation:

- These are two basic modes of operation of 8255. I/O mode and Bit Set-Reset mode (BSR).
- In I/O mode, the 8255 ports work as programmable I/O ports, while in BSR mode only port C (PC0-PC7) can be used to set or reset its individual port bits.

- Under the I/O mode of operation, further there are three modes of operation of 8255, so as to support different types of applications, mode 0, mode 1 and mode 2.
- BSR Mode: In this mode any of the 8-bits of port C can be set or reset depending on D0 of the control word. The bit to be set or reset is selected by bit select flags D3, D2 and D1 of the CWR as given in table.

I/O Modes:

1. Mode 0 (Basic I/O mode):

This mode is also called as basic input/output Mode. This mode provides simple input and output capabilities using each of the threeports. Data can be simply read from and written to the input and output portsrespectively, after appropriate initialization.

D ₃	D ₂	D ₁	Selected bits of port C
0	0	0	D ₀
0	0	1	D ₁
0	1	0	D ₂
0	1	1	D ₃
1	0	0	D ₄
1	0	1	D ₅
1	1	0	D ₆
1	1	1	D ₇

BSR Mode : CWR Format

Figure 4.1.4 Control word register of 8255A

[Source: "Microprocessor Architecture Programming and Application" by R.S. Gaonkar, page-]

- Two 8-bit ports (port A and port B) and two 4-bit ports (port C upper and lower) are available. The two 4-bit ports can be combined used as a third 8-bit port.
- Any port can be used as an input or output port.
- Output ports are latched. Input ports are not latched.
- A maximum of four ports are available so that overall 16 I/O configurations are possible.
- All these modes can be selected by programming a register internal to 8255known as CWR.

- The control word register has two formats. The first format is valid for I/O modes of operation, i.e. modes 0, mode 1 and mode 2 while the second format is valid for bit set/reset (BSR) mode of operation.

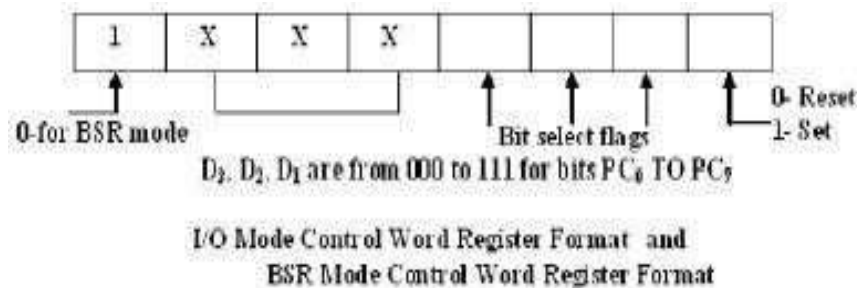


Figure 4.1.5 Control word of 8255A

[Source: "Microprocessor Architecture Programming and Application" by R.S. Gaonkar, page-]

2. Mode 1: (Strobed input/output mode)

In this mode the handshaking control the input and output action of the specified port. Port C lines PC0-PC2, provide strobe or handshake lines for port B. This group which includes port B and PC0-PC2 is called as group B for Strobed data input/output. Port C lines PC3-PC5 provides strobe lines for port A. This group including port A and PC3-PC5 from group A. Thus port C is utilized for generating handshake signals.

- Two groups – group A and group B are available for strobed data transfer.
- Each group contains one 8-bit data I/O port and one 4-bit control/data port.
- The 8-bit data port can be either used as input and output port. The inputs and outputs both are latched.
- Out of 8-bit port C, PC0-PC2 are used to generate control signals for port B and PC3-PC5 are used to generate control signals for port A. the lines PC6, PC7 may be used as independent data lines.
- OBF (Output buffer full) – This status signal, whenever falls to low, indicates that CPU has written data to the specified output port. The OBF flip-flop will be set by a rising edge of WR signal and reset by a low going edge at the ACK input.
- ACK (Acknowledge input) – ACK signal acts as an acknowledgement to be given by an output device. ACK signal, whenever low, informs the CPU that the data

transferred by the CPU to the output device through the port is received by the output device.

- INTR (Interrupt request) – Thus an output signal that can be used to interrupt the CPU when an output device acknowledges the data received from the CPU. INTR is set when ACK, OBF and INTE are 1. It is reset by a Falling edge on WR input. The INTEA and INTEB flags are controlled by the bit set- reset mode of PC6 and PC2 respectively.

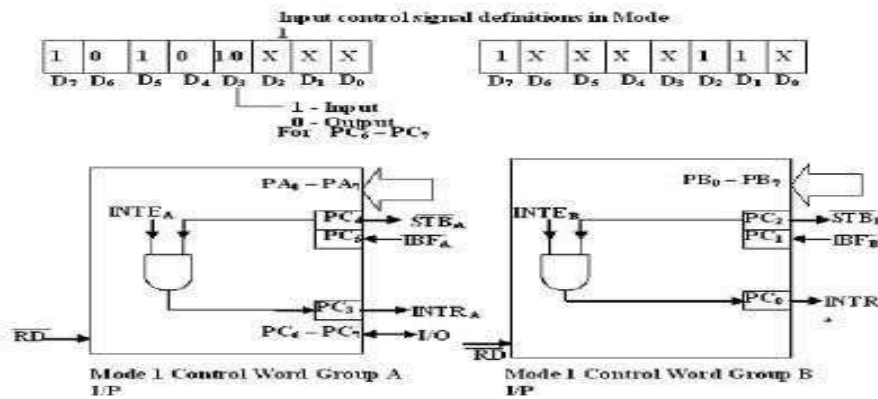


Figure 4.1.6 Group A and Group B control of 8255A

[Source: "Microprocessor Architecture Programming and Application" by R.S. Gaonkar, page-]

3.Mode 2 (Strobed bidirectional I/O):

This mode of operation of 8255 is also called as strobed bidirectional I/O. This mode of operation provides 8255 with additional features for communicating with a peripheral device on an 8-bit data bus. Handshaking signals are provided to maintain proper data flow and synchronization between the data transmitter and receiver. The interrupt generation and other functions are similar to mode1. In this mode, 8255 is a bidirectional 8-bit port with handshake signals. The Rd and WR signals decide whether the 8255 is going to operate as an input port or output port.

- The single 8-bit port in group A is available.
- The 8-bit port is bidirectional and additionally a 5-bit control port is available.
- Three I/O lines are available at port C.(PC2 – PC0)
- Inputs and outputs are both latched.
- The 5-bit control port C (PC3-PC7) is used for generating/ accepting handshake signals for the 8-bit data transfer on port A.

- INTR – (Interrupt request) As in mode 1, this control signal is active high and is used to interrupt the microprocessor to ask for transfer of the next data byte to/from it. This signal is used for input (read) as well as output (write) operations.

Control Signals for Output operations:

- OBF (Output buffer full) – This signal, when falls to low level, indicates that the CPU has written data to port A.
- ACK (Acknowledge) This control input, when falls to logic low level, acknowledges that the previous data byte is received by the destination and next byte may be sent by the processor. This signal enables the internal tristate buffers to send the next data byte on port A.
- INTE1 (A flag associated with OBF) This can be controlled by bit set/reset mode with PC6.
- STB (Strobe input) a low on this line is used to strobe in the data into the input Latches of 8255.
- IBF (Input buffer full) when the data is loaded into input buffer, this signal rises to logic „1“. This can be used as an acknowledge that the data has been received by the receiver.
- The waveforms in fig show the operation in Mode 2 for output as well as input port. Note: WR must occur before ACK and STB must be activated before RD.
- The following fig shows a schematic diagram containing an 8-bit bidirectional port, 5-bit control port and the relation of INTR with the control pins. Port B can either be set to Mode 0 or 1 with port A(Group A) is in Mode 2.
- Mode 2 is not available for port B. The following fig shows the control word.
- The INTR goes high only if IBF, INTE2, STB and RD go high or OBF, INTE1, ACK and WR go high. The port C can be read to know the status of the peripheral device, in terms of the control signals, using the normal I/O instructions

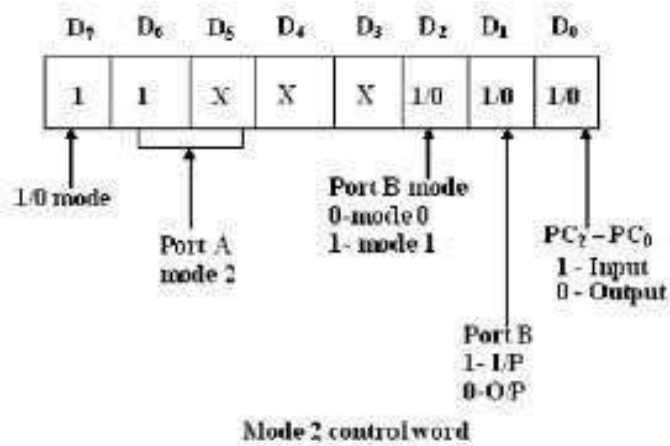


Figure 4.1.7 Control word

[Source: "Microprocessor Architecture Programming and Application" by R.S. Gaonkar, page-]

www.binils.com

4.2 INTEL 8259A Programmable Interrupt Controller

The 8259A is a programmable interrupt controller designed to work with Intel microprocessor 8080 A, 8085, 8086, 8088. The 8259 A interrupt controller can

- 1) Handle eight interrupt inputs. This is equivalent to providing eight interrupt pins on the processor in place of one INTR/INT pin.
- 2) Vector an interrupt request anywhere in the memory map. However, all the eight interrupt are spaced at the interval of either four or eight location. This eliminates the majordrawback, 8085 interrupt, in which all interrupts are vectored to memory location on page 00H.
- 3) Resolve eight levels of interrupt priorities in a variety of modes.
- 4) Mask each interrupt request individually.
- 5) Read the status of pending interrupts, in service interrupts, and masked interrupts.
- 6) Be set up to accept either the level triggered or edge triggered interrupt request.
- 7) Mine 8259 as can be cascade in a master slave configuration to handle 64 interrupt inputs.

The 8259 A is contained in a 28-element in line package that requires only a compatible with 8259. The main difference between the two is that the 8259 A can be used with Intel 8086/8088 processor.

 


Figure 4.2.1 Pin diagram of 8259A

[Source: "Microprocessor Architecture Programming and Application" by R.S. Gaonkar, page-]

It also induces additional features such as level triggered mode, buffered mode and automatic end of interrupt mode. The pin diagram and interval block diagram is shown in 4.2.1.

Symbol	Pin No.	Type	Name and Function
VCC	2 8	I	SUPPLY: + 5V Supply.
GND	1 4	I	GROUND
CS	1	I	CHIP SELECT: A low on this pin enables RD and WR communication between the CPU and the 8259A. INTA functions are independent of CS
WR	2	I	WRITE: A low on this pin when CS is low enables The 8259A to accept command words from the CPU.
RD	3	I	READ: A low on this pin when CS is low enables the 8259A to release status onto the data bus for the CPU.
D7–D0	4 –11	I/O	BIDIRECTIONAL DATA BUS: Control, status and interrupt-vector information is transferred via this bus.
CAS0–CAS2	12, 13, 15	I/O	CASCADE LINES: The CAS lines form a private 8259A bus to control a multiple 8259A structure. These pins are outputs for a master 8259A and Inputs slave 8259A.

The 8259 A has eight interrupt request inputs, TR2 IR0. The 8259 A uses its INT output to interrupt the 8085A via INTR pin. The 8259A receives interrupt acknowledge pulses from the at its input. Vector address used by the 8085 A to transfer control to the service subroutine of the interrupting device, is provided by the 8259 A on the data bus. The 8259A is a programmable device that must be initialized by command words sent by the. After initialization, the 8259 A mode of operation can be changed by operation command words from the. The descriptions of various blocks are,

Data bus buffer - This 3- state, bidirectional 8-bit buffer is used to interface the 8259A to the system data bus. Control words and status information are transferred through the data bus buffer.

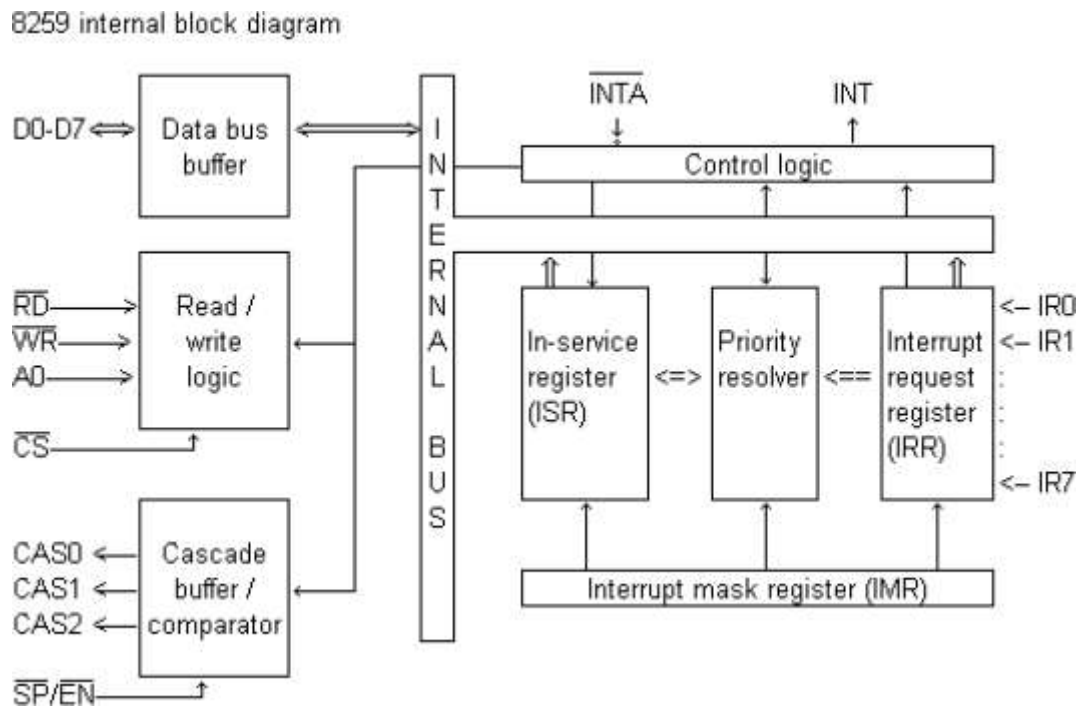


Figure 4.2.2 Architecture of 8259A

[Source: "Microprocessor Architecture Programming and Application" by R.S. Gaonkar, page-]

Read/Write & control logic - The function of this block is to accept OUTPUT commands from the CPU. It contains the initialization command word (ICW) register and operation command word (OCW) register which store the various control formats for device operation. This function block also allows the status of 8159A to be transferred to the data bus.

Interrupt request register (IRR) - IRR stores all the interrupt inputs that are requesting service. Basically, it keeps track of which interrupt inputs are asking for service. If an interrupt input is unmasked, and has an interrupt signal on it, then the corresponding bit in the IRR will be set.

Interrupt mask register (IMR) -The IMR is used to disable (Mask) or enable (Unmask) individual interrupt inputs. Each bit in this register corresponds to the interrupt input with the same number. The IMR operation on the IRR. Masking of higher priority input will not affect the interrupt request lines of lower priority. To unmask any interrupt the corresponding bit is set „0“.

In service register (ISR) - The in-service registers keeps tracks of which interrupt inputs are currently being serviced. For each input that is currently being serviced the corresponding bit will be set in the in-service register. Each of these 3-reg can be read as status reg.

Priority Resolver -This logic block determines the priorities of the set in the IRR. The highest priority is selected and strobed into the corresponding bit of the ISR during pulse.

Cascade buffer/comparator - This function blocks stores and compare the IDS of all 8259A's in the reg. The associated 3-I/O pins (CAS0-CAS2) are outputs when 8259A is used a master. Master and are inputs when 8259A is used as a slave. As a master, the 8259A sends the ID of the interrupting slave device onto the cas2-cas0. The slave thus selected will send its pre-programmed subroutine address on to the data bus during the next one or two successive pulses.

www.binils.com

4.4 8279- Programmable Keyboard/Display Controller

8279 programmable keyboard/display controller is designed by Intel that interfaces a keyboard with the CPU. The keyboard first scans the keyboard and identifies if any key has been pressed. It then sends their relative response of the pressed key to the CPU and vice-a-versa.

The Keyboard can be interfaced either in the interrupt or the polled mode. In the Interrupt mode, the processor is requested service only if any key is pressed, otherwise the CPU will continue with its main task. In the Polled mode, the CPU periodically reads an internal flag of 8279 to check whether any key is pressed or not with key pressure.

The keyboard consists of maximum 64 keys, which are interfaced with the CPU by using the key-codes. These key-codes are de-bounced and stored in an 8-byte FIFO/RAM, which can be accessed by the CPU. If more than 8 characters are entered in the FIFO, then it means more than eight keys are pressed at a time. This is when the overrun status is set.

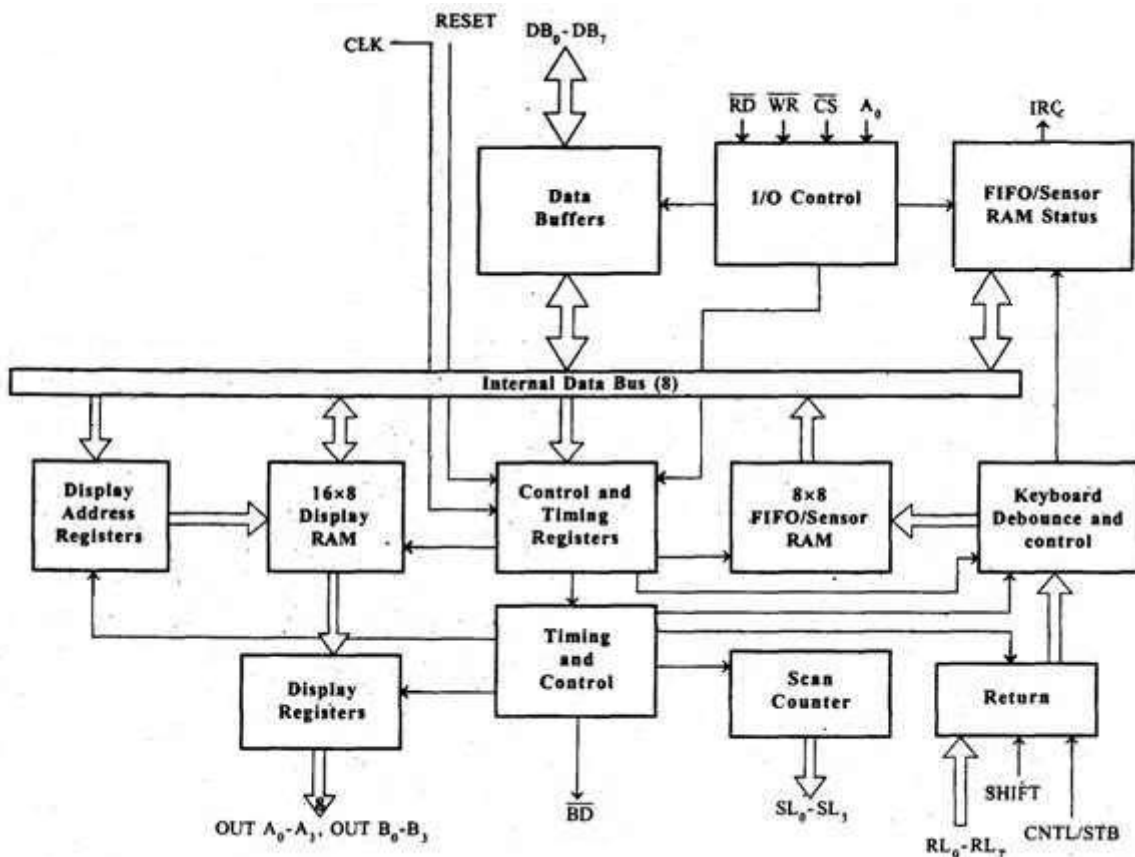


Figure 4.4.1 Architecture of 8259

[Source: "Microprocessor Architecture Programming and Application" by R.S. Gaonkar, page-]

If a FIFO contains a valid key entry, then the CPU is interrupted in an interrupt mode else the CPU checks the status in polling to read the entry. Once the CPU reads a key entry, then FIFO is updated, and the key entry is pushed out of the FIFO to generate space for new entries.

I/O Control and Data Buffer

This unit controls the flow of data through the microprocessor. It is enabled only when D is low. Its data buffer interfaces the external bus of the system with the internal bus of the microprocessor. The pins A0, RD, and WR are used for command, status or data read/write operations.

Control and Timing Register and Timing Control

This unit contains registers to store the keyboard, display modes, and other operations as programmed by the CPU. The timing and control unit handles the timings for the operation of the circuit.

Scan Counter

It has two modes i.e. Encoded mode and Decoded mode. In the encoded mode, the counter provides the binary count that is to be externally decoded to provide the scan lines for the keyboard and display. In the decoded scan mode, the counter internally decodes the least significant 2 bits and provides a decoded 1 out of 4 scan on SL0-SL3.

Return Buffers, Keyboard Debounce, and Control

This unit first scans the key closure row-wise, if found the keyboard debounce unit debounces the key entry. In case, the same key is detected, then the code of that key is directly transferred to the sensor RAM along with SHIFT & CONTROL key status.

FIFO/Sensor RAM and Status Logic

This unit acts as 8-byte first-in-first-out (FIFO) RAM where the key code of every pressed key is entered into the RAM as per their sequence. The status logic generates an interrupt request after each FIFO read operation till the FIFO gets empty.

In the scanned sensor matrix mode, this unit acts as sensor RAM where its each row is loaded with the status of their corresponding row of sensors into the matrix. When the sensor changes its state, the IRQ line changes to high and interrupts the CPU.

Display Address Registers and Display RAM

This unit consists of display address registers which holds the addresses of the word currently read/written by the CPU to/from the display RAM.

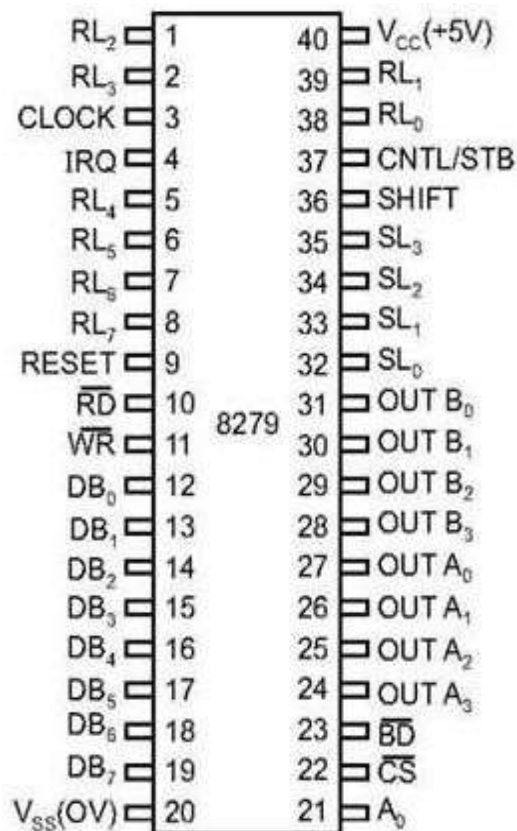


Figure 4.4.2 Pin diagram of 8259

[Source: "Microprocessor Architecture Programming and Application" by R.S. Gaonkar, page-]

Data Bus Lines, DB0 - DB7

These are 8 bidirectional data bus lines used to transfer the data to/from the CPU.

CLK

The clock input is used to generate internal timings required by the microprocessor.

RESET

As the name suggests this pin is used to reset the microprocessor.

CS Chip Select

When this pin is set to low, it allows read/write operations, else this pin should be set to high.

A0

This pin indicates the transfer of command/status information. When it is low, it indicates the transfer of data.

RD, WR

This Read/Write pin enables the data buffer to send/receive data over the data bus.

IRQ

This interrupt output line goes high when there is data in the FIFO sensor RAM. The interrupt line goes low with each FIFO RAM read operation. However, if the FIFO RAM further contains any key-code entry to be read by the CPU, this pin again goes high to generate an interrupt to the CPU.

Vss, Vcc

These are the ground and power supply lines of the microprocessor.

SL0 – SL3

These are the scan lines used to scan the keyboard matrix and display the digits. These lines can be programmed as encoded or decoded, using the mode control register.

RL0 – RL7

These are the Return Lines which are connected to one terminal of keys, while the other terminal of the keys is connected to the decoded scan lines. These lines are set to 0 when any key is pressed.

SHIFT

The Shift input line status is stored along with every key code in FIFO in the scanned keyboard mode. Till it is pulled low with a key closure, it is pulled up internally to keep it high

CNTL/STB - CONTROL/STROBED I/P Mode

In the keyboard mode, this line is used as a control input and stored in FIFO on a key closure. The line is a strobe line that enters the data into FIFO RAM, in the strobed input mode. It has an internal pull up. The line is pulled down with a key closure.

BD

It stands for blank display. It is used to blank the display during digit switching.

OUTA0 – OUTA3 and OUTB0 – OUTB3

These are the output ports for two 16x4 or one 16x8 internal display refresh registers. The data from these lines is synchronized with the scan lines to scan the display and the keyboard.

Operational Modes of 8279

There are two modes of operation on 8279

- Input Mode
- Output Mode.

Input Mode

This mode deals with the input given by the keyboard and this mode is further classified into 3 modes.

Scanned Keyboard Mode – In this mode, the key matrix can be interfaced using either encoded or decoded scans. In the encoded scan, an 8×8 keyboard or in the decoded scan, a 4×8 keyboard can be interfaced. The code of key pressed with SHIFT and CONTROL status is stored into the FIFO RAM.

Scanned Sensor Matrix – In this mode, a sensor array can be interfaced with the processor using either encoder or decoder scans. In the encoder scan, 8×8 sensor matrix or with decoder scan 4×8 sensor matrix can be interfaced.

Strobed Input – In this mode, when the control line is set to 0, the data on the return lines is stored in the FIFO byte by byte.

Output Mode

This mode deals with display-related operations. This mode is further classified into two output modes.

Display Scan – This mode allows 8/16 character multiplexed displays to be organized as dual 4-bit/single 8-bit display units.

Display Entry – This mode allows the data to be entered for display either from the right side/left side.

4.5 ADC and DAC Interfacing:

The Analog to Digital Conversion is a quantizing process. Here the analog signal is represented by equivalent binary states. The A/D converters can be classified into two groups based on their conversion techniques.

In the first technique it compares given analog signal with the initially generated equivalent signal. In this technique, it includes successive approximation, counter and flash type converters. In another technique it determines the changing of analog signals into time or frequency. This process includes integrator-converters and voltage-to-frequency converters. The first process is faster but less accurate, the second one is more accurate. As the first process uses flash type, so it is expensive and difficult to design for high accuracy.

ADC 0808/0809 Chip

The ADC 0808/0809 is an 8-bit analog to digital converter. It has 8 channel multiplexer to interface with the microprocessor.

This chip is popular and widely used ADC. ADC 0808/0809 is a monolithic CMOS device. This device uses successive approximation technique to convert analog signal to digital form. One of the main advantage of this chip is that it does not require any external zero and full scale adjustment, only +5V DC supply is sufficient.

Let us see some good features of ADC 0808/0809:

- The conversion speed is much higher
- The accuracy is also high
- It has minimal temperature dependence
- Excellent long term accuracy and repeatability
- Less power consumption

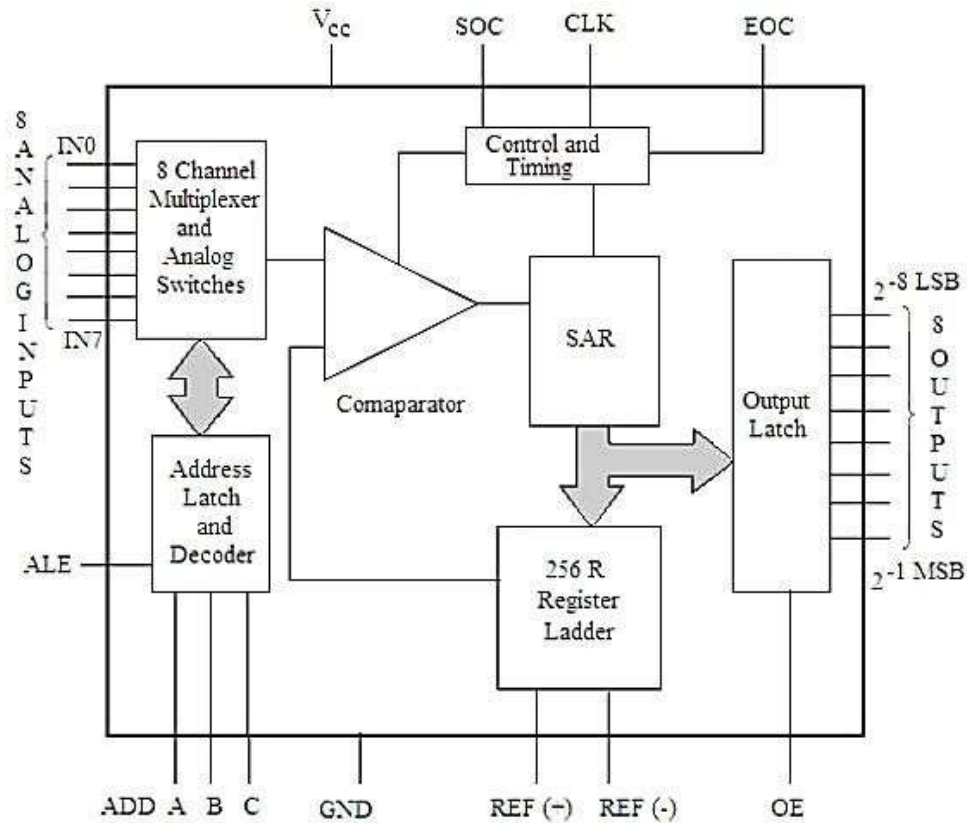


Figure 4.4.1 Architecture of ADC

[Source: "Microprocessor Architecture Programming and Application" by R.S. Gaonkar, page-]

Interfacing ADC with 8085 Microprocessor

To interface the ADC with 8085, we need 8255 Programmable Peripheral Interface chip with it. Let us see the circuit diagram of connecting 8085, 8255 and the ADC converter.

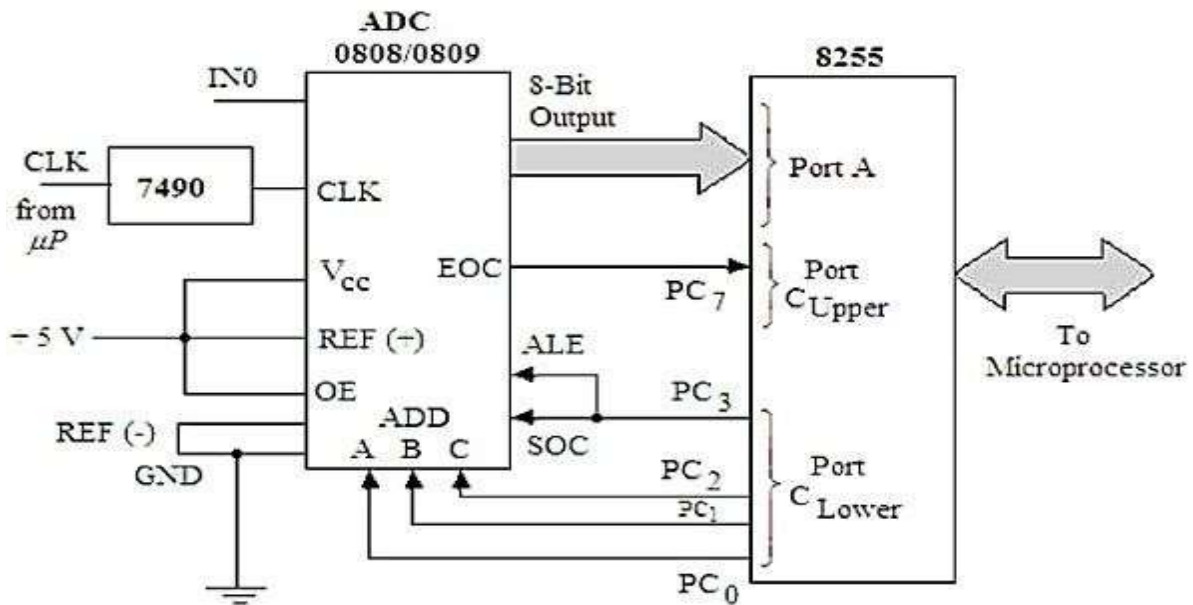


Figure 4.4.1 Interfacing ADC with 8085 Microprocessor

[Source: "Microprocessor Architecture Programming and Application" by R.S. Gaonkar, page-]

The PortA of 8255 chip is used as the input port. The PC7 pin of Port Cupper is connected to the End of Conversion (EOC) Pin of the analog to digital converter. This port is also used as input port. The Clower port is used as output port. The PC2-0 lines are connected to three address pins of this chip to select input channels. The PC3 pin is connected to the Start of Conversion (SOC) pin and ALE pin of ADC 0808/0809.

Now let us see a program to generate digital signal from analog data. We are using IN0 as input pin, so the pin selection value will be 00H

MVI A, 98H ; Set Port A and Cupper as input, CLower as output

OUT 03H ; Write control word 8255-I to control Wordregister

XRA A ; Clear the accumulator

OUT 02H ; Send the content of Acc to Port Clower to select

IN0

MVI A, 08H ; Load the accumulator with 08H

OUT 02H ; ALE and SOC will be 0

XRA A ; Clear the accumulator

OUT 02H ; ALE and SOC will be low.

READ: IN 02H ; Read from EOC (PC7)

RAL ; Rotate left to check C7 is 1.

JNC READ ; If C7 is not 1, go to READ

IN 00H ; Read digital output of ADC

STA 8000H ; Save result at 8000H

HLT ; Stop the program

DAC Interfacing with 8085 Microprocessor

- DAC 0800 Features
- To convert the digital signal to analog signal a Digital-to-Analog Converter (DAC) has to be employed.
- The DAC will accept a digital (binary) input and convert to analog voltage or current.

- Every DAC will have "n" input lines and an analog output.
- The DAC require a reference analog voltage (V_{ref}) or current (I_{ref}) source.
- The smallest possible analog value that can be represented by the n-bit binary code is called resolution.
- The resolution of DAC with n-bit binary input is $1/2^n$ of reference analog value.
- The DAC0800 is an 8-bit, high speed, current output DAC with a typical settling time (conversion time) of 100 ns.
- It produces complementary current output, which can be converted to voltage by using simple resistor load.
- The DAC0800 require a positive and a negative supply voltage in the range of $\pm 5V$ to $\pm 18V$.

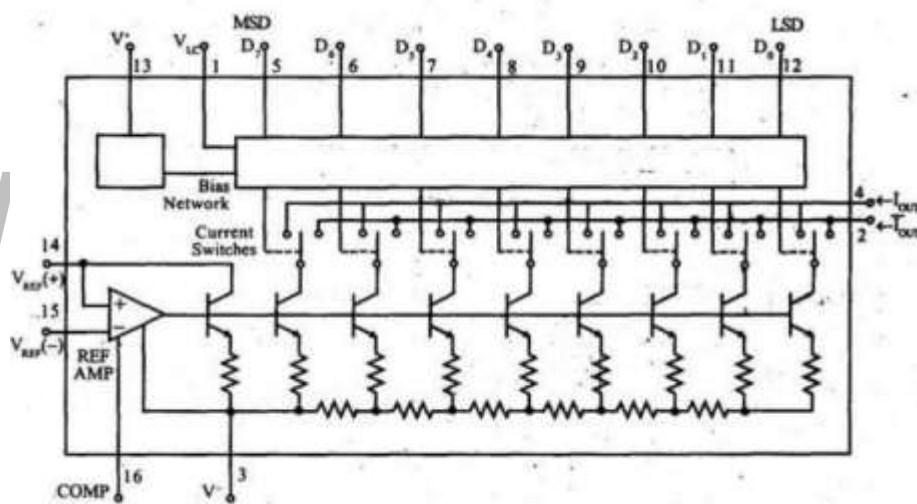


Fig 3.17 Circuit Diagram of DAC 0800

Figure 4.4.1 Circuit diagram of DAC 0800

[Source: "Microprocessor Architecture Programming and Application" by R.S. Gaonkar, page-]

- It can be directly interfaced with TTL, CMOS, PMOS and other logic families.
- For TTL input, the threshold pin should be tied to ground ($V_{LC} = 0V$).
- The reference voltage and the digital input will decide the analog output current, which can be converted to a voltage by simply connecting a resistor to output terminal or by using an op-amp I to V converter.
- The DAC0800 is available as a 16-pin IC in DIP.

Square Wave Generation Using DAC 0800:

ADDRESS	LABEL	MNEMONICS	OPCODE
	START	MVI A,00H OUT C8 CALL DELAY MVI A,FF OUT C8 CALL DELAY JMP START MVI B,05H MVI C,FF	
	DELAY	DCR C	
	L2	JNZ L1 DCR B	
	L1	JNL L2 RET	

)m