

Basics of Electronics and Microprocessor Engineering

Important 10mark questions

Unit I

1. Explain the forward and reverse bias characteristics of PN junction diode.
2. Explain in detail about how transistor act as switch.

Unit II

1. Explain how an Op-Amp is used as comparator and buffer in detail.
2. Explain the characteristics of an operational amplifier in detail.

Unit III

1. Draw the logic diagram of full adder and explain in detail.
2. Explain in detail about Mod n counter.

Unit IV

1. Draw the block diagram of 8051 microcontroller and explain.
2. Explain the various addressing modes of 8051 in detail.

Unit V

1. Explain the various modes of operation of 8255 IC in detail.
2. Explain sensor interfacing with 8051 in detail.